

Q. A 220V dc machine has an Armature resistance of 1Ω , if full load current is 20 Amp. the diff. of induced voltage, when the machine is running as a motor and generator is—

Solⁿ

as motor

$$E = V - I_a R_a$$

$$= 220 - 20 \cdot 1$$

$$= \underline{\underline{200V}}$$

as generator

$$E = V + I_a R_a$$

$$= 220 + 20 \cdot 1$$

$$= \underline{\underline{240V}}$$

diff. of induced voltage is \rightarrow 40V

Q. the current drawn by 220V dc motor of $R_a = 0.5\Omega$ & back emf 200V is \rightarrow ?

Solⁿ

in motor

$$E_b = V - I_a R_a$$

$$I_a = \frac{-E_b + V}{R_a} = \frac{V - E_b}{R_a}$$

$$= \frac{220V - 200}{0.5} = \frac{200}{0.5}$$

$$I_a = 40 \text{ Amp.}$$

Q. A 400V dc shunt motor takes 5 A at no load
 $R_a = 0.5$, $R_f = 2\ \Omega$, what is ratio of speed from full load to no-load when dc shunt motor takes 50 Amp. on full load?

Solⁿ

$$I_{sh} = \frac{400}{200} = 2 \text{ Amp}$$


$$\therefore I_a = 3$$

$$E_b = V - I_a R_a$$

$$= 400 - 3 \times 0.5$$

$$= 400 - 1.5$$

$$= \underline{398.5 \text{ V}}$$

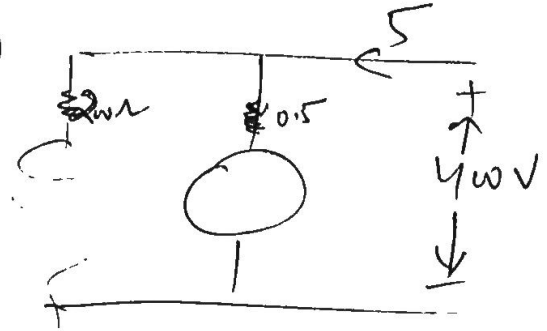

at full load

$$I_a = 48 \text{ amp}$$

$$E_b = 400 - 48 \times 0.5$$

$$= \underline{376 \text{ V}}$$

ratio of speed from no load to full load.


$$\left\{ N \times \frac{E_b}{\Phi} \right\} = \text{Const.}$$

$$\frac{N_1}{N_2} = \frac{E_1}{E_2}$$

$$\frac{N_{noL}}{N_{FL}} = \frac{398.5}{376}$$

$$\Rightarrow \frac{N_{FL}}{N_{NL}} = 0.94$$

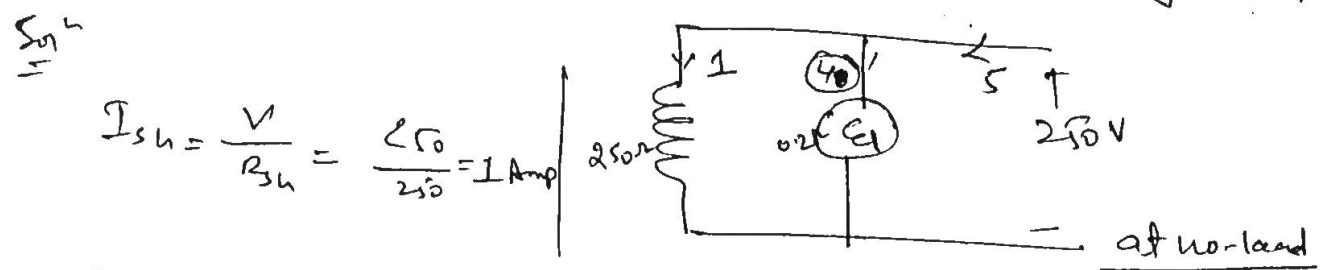Q.2. A 250V, shunt motor on no-load run at 1000 rpm and take 5 amp. the total armature & shunt resistance are resp. $0.2 \Omega + 250 \Omega$. Calculate speed when loaded & taking a current of 50 amp., if the armature reaction reduce the field by 3%.



$$I_{sh} = \frac{V}{R_{sh}} = \frac{250}{250} = 1 \text{ Amp}$$

$$E_1 = V - I_a R_a$$

$$= 250 - 4 \times 0.2$$

$$= 250 - 0.8$$

$$= \underline{249.2 \text{ V}}$$

$$E_2 = V - I_a R_a$$


$$= 250 - (49 \times 0.2)$$

$$= \underline{240.2 \text{ Volt}}$$

By ~~emf~~ formula

$$\frac{E_1}{E_2} = \frac{N_1 \phi_1}{N_2 \phi_2}$$
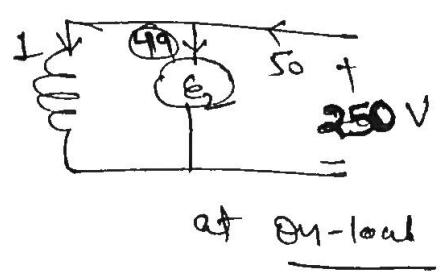
$$= \frac{249.2}{240.2} = \frac{1000 \times \phi}{N_2 \times 0.97 \phi}$$



$$N_2 = 993.69 \text{ rpm}$$

Q. the armature resistance of a 200V shunt motor is 0.4Ω & no-load armature current is 2 amp. when loaded taking an armature current of 50 amp., the speed is 1200 rpm find the approx. no-load speed.


$$\therefore \left(\frac{E_1}{E_2} = \frac{N_1}{N_2} \right)$$

$$\begin{aligned} E_1 &= V - I_a R_{NL} \\ &= 200 - 2 \times 0.4 \\ &= 200 - 0.8 \\ &= \underline{\underline{199.2 \text{ V}}} \end{aligned}$$

$$\begin{aligned} E_2 &= V - I_a R_{FL} \\ &= 200 - (50 \times 0.4) = \underline{\underline{180 \text{ V}}} \end{aligned}$$

$$\therefore \left(\frac{199.2}{180} = \frac{N_1}{1200} \right)$$
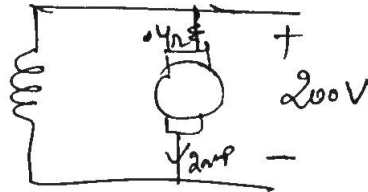
$$\therefore \boxed{N_1 = 1328 \text{ rpm}}$$



(at no-load)

$$\begin{cases} E_1 = k \phi N_1 \\ E_2 = k \phi N_2 \end{cases}$$

