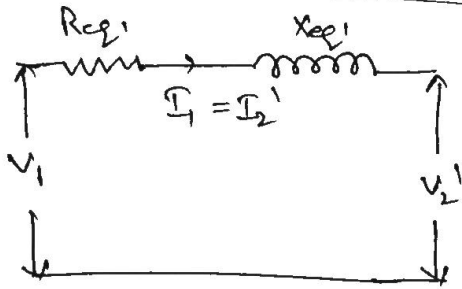



Voltage Regulation



It is
 → diff b/w No-load voltage to full load v_{tg} respect to no-load v_{tg}.

$$* V.R. = \frac{N.L. v_{tg} - F.L. v_{tg}}{\text{full load } v_{tg}}$$
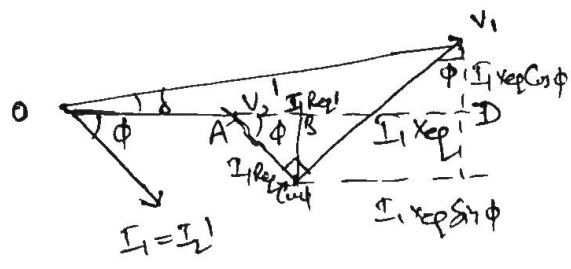
$$\left(Reg. = \frac{V_1 - V_2'}{V_2'} \right)$$



$$OD = V_1 \cos \delta$$

$$V_1 \approx V_1 \cos \delta$$

$$\boxed{OD = V_1}$$

No-load v_{tg}

OA → full load v_{tg}

$$V_1 - V_2' = OD - OA = AD$$

$$= AB + BD$$

$$= I_1 R_{ep1} \cos \phi + I_1 X_{ep1} \sin \phi$$

$$\left[\underline{Reg.} = \frac{I_1 R_{ep1} \cos \phi + I_1 X_{ep1} \sin \phi}{V_2'} \right] \rightarrow \text{lagging}$$

↳ lagging P.f.

$$\left[\text{Regulation} = \frac{I_1 R_{ep1} \cos \phi - I_1 X_{ep1} \sin \phi}{V_2'} \right] \rightarrow \text{leading.}$$

Condⁿ for Zero v_r Regulation

* Possible only on leading P.F. ✓

* -ve v_r possible only on leading P.F. ✓

$$0 = \frac{I_1 R_{eq1} \cos \phi - I_1 X_{eq1} \sin \phi}{V_2'}$$

$$I_1 X_{eq1} \sin \phi = I_1 R_{eq1} \cos \phi$$

$$\frac{\sin \phi}{\cos \phi} = \frac{R_{eq1}}{X_{eq1}}$$

$$\tan \phi = \frac{R_{eq1}}{X_{eq1}}$$

* Condⁿ for max. v_r →

$$\phi = \tan^{-1} \left(\frac{X_{eq1}}{R_{eq1}} \right)$$

Condⁿ for
Z.v.r.


$$\phi = \tan^{-1} \left(\frac{R_{eq1}}{X_{eq1}} \right)$$

$$\text{Regulation} = \frac{I_1 R_{eq1} \cos \phi \pm I_1 X_{eq1} \sin \phi}{V_2'}$$

$$= \frac{I_1 R_{eq1}}{V_2'} \cos \phi \pm \frac{I_1 X_{eq1}}{V_2'} \sin \phi$$


$$\checkmark \text{ Reg.} = \left[R_{eq1} \cos \phi \pm X_{eq1} \sin \phi \right] \begin{cases} * + \rightarrow \text{lag} \\ * - \rightarrow \text{lead.} \end{cases}$$

Open Circuit Test
 ↳ find core/iron loss

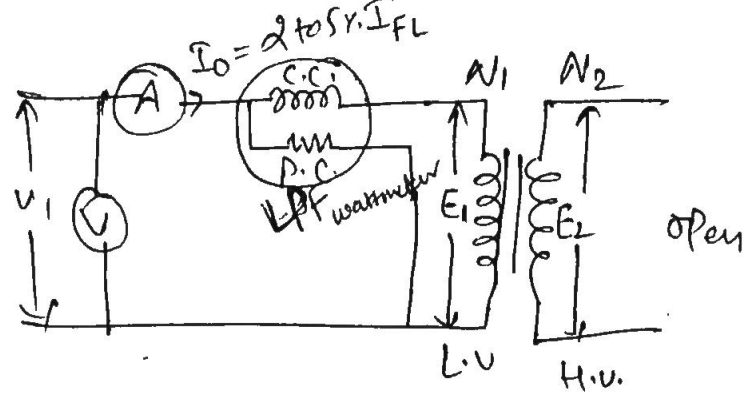

Wattmeter Reading

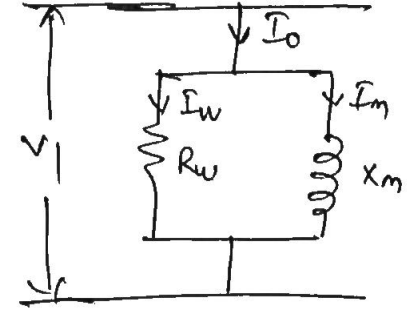
$W = V_1 I_w \text{ Watt}$
 $[W = V_1 I_0 \cos \phi_0 \text{ watt}]$



$\phi_0 \rightarrow 75^\circ$
 $\< 90^\circ$

$I_0 = \sqrt{I_w^2 + I_m^2}$
 $I_w = I_0 \cos \phi_0$
 $I_m = I_0 \sin \phi_0$


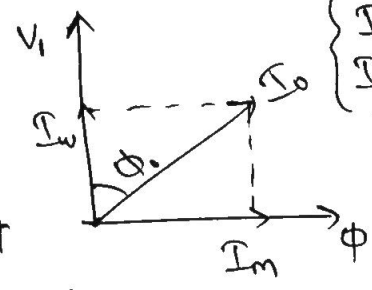
Reactive Power = $V_1 I_m$ VAR
 $= V_1 I_0 \sin \phi_0 \text{ V.A.R.}$



$I_w \rightarrow$ watt full component
 $I_m \rightarrow$ magnetising component.

Short Circuit Test

↳ Copper loss / variable loss

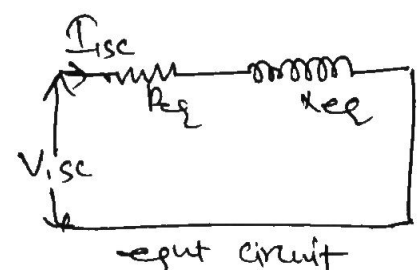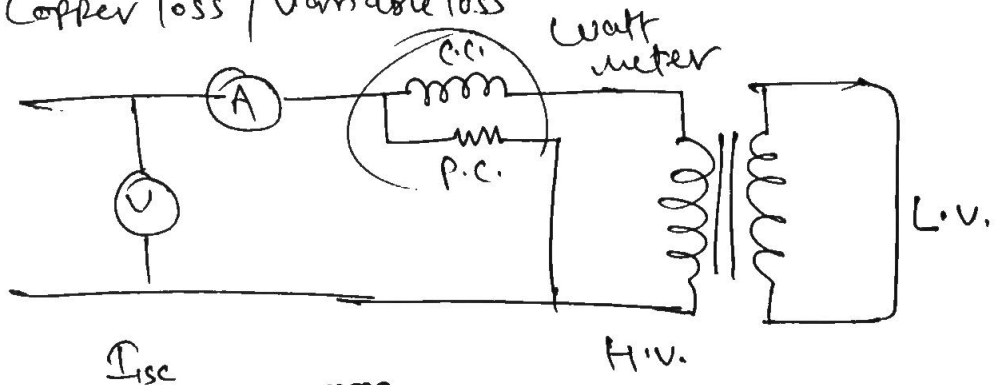

$\{ \text{Cu loss} = V_{1sc} I_{sc} \cos \phi_{sc} \}$

Efficiency: (η)

$$\eta = \frac{\text{O/P Power}}{\text{S/P Power}} = \frac{\text{O/P Power}}{\text{O/P Power} + \text{Losses}}$$

$$\text{O/P Power} = V_2 I_2 \cos \phi \text{ watt}$$

$$\text{Iron loss } (P_i) = P_i \text{ watt}$$

$$\text{Cu loss} = P_c \text{ watt}$$

$$\eta = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_i + P_c} \rightarrow \text{for full load} \quad \text{--- (1)}$$

if $m \rightarrow$ load ratio

$$m = 1 \text{ (full load)}$$

$$m = 1/2 \text{ (half load)}$$

$$m = 1/4 \text{ (one fourth load)}$$

$$\eta_{atm} = \frac{m \cdot V_2 I_2 \cos \phi}{m V_2 I_2 \cos \phi + P_i + m^2 P_c} \quad \text{--- (2)}$$

$S \rightarrow V_2 I_2$ (Rating)

$$\left\{ \eta_{atm} = \frac{m S \cos \phi}{m S \cos \phi + P_i + m^2 P_c} \right\} \quad \text{--- (3)}$$

Condⁿ for max. efficiency

$$\eta = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_i + P_c}$$
$$= \frac{V_2 I_2 \cos \phi}{\left[V_2 \cos \phi + \frac{P_i}{I_2} + I_2 R_{eq} \right]}$$

for max. $\eta \rightarrow$


$$D = V_2 \cos \phi + \frac{P_i}{I_2} + I_2 R_{eq}$$

$$\frac{dD}{dI} = 0$$

$$0 - \frac{P_i}{I_2^2} + R_{eq} = 0$$

$$P_i = I_2^2 R_{eq}$$
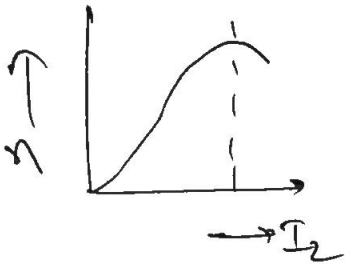
$$* \boxed{P_i = P_c} \quad \text{OR} \quad \left(\text{Core loss} = \text{Cu loss} \right)^*$$



$$I_{2m} = I_{2fl} \times \sqrt{\frac{P_i}{P_c}}$$

$$V_2 I_{2m} = V_2 I_{2fl} \times \sqrt{\frac{P_i}{P_c}}$$

$$\left(S_m = S_{fl} \times \sqrt{\frac{P_i}{P_c}} \right)$$

$$\boxed{P_i = P_c}$$

$$P_i = m^2 P_c$$

load ratio at
max. efficiency $m = \sqrt{\frac{P_i}{P_c}}$

$$\begin{aligned} P_i &= 300 \text{ W} \\ P_c &= 300 \text{ W} \end{aligned}$$

for max eff. ~~at~~
total load $\rightarrow ?$

$$\boxed{P_T = 600 \text{ watt}}$$