
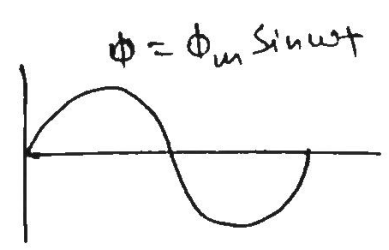


$$\left(\phi = \frac{V}{S} \right)$$

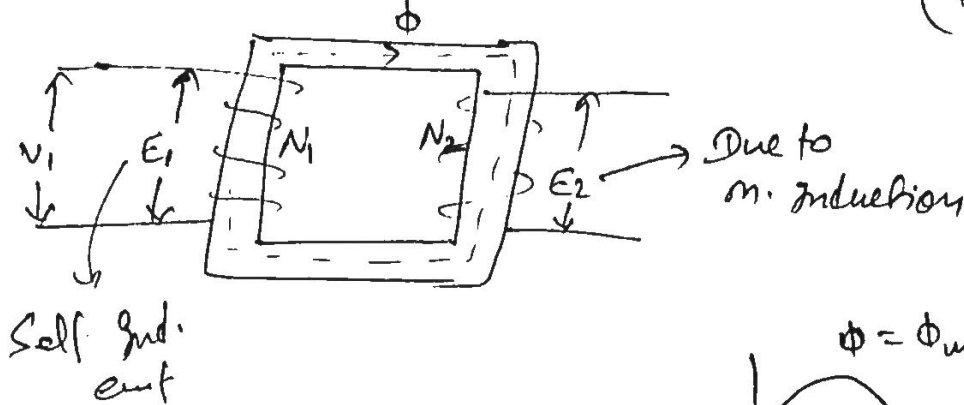

Emf eqⁿ

$$\phi = \phi_m \sin \omega t \quad \text{--- (1)}$$

$$e_1 = -N_1 \frac{d\phi}{dt}$$

$$e_1 = -N_1 \frac{d(\phi_m \sin \omega t)}{dt}$$


$$= -N_1 \phi_m \cos \omega t \cdot \omega$$

$$= \frac{N_1 \phi_m \omega \sin(\omega t - 90^\circ)}{\hookrightarrow \text{max. v.}}$$

$$e_1 \text{ (rms)} = \frac{N_1 \phi_m \omega}{\sqrt{2}}$$

$$= \frac{2\pi f N_1 \phi_m}{\sqrt{2}}$$
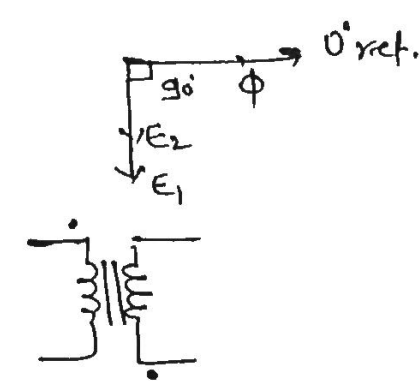
$$\boxed{E_1 = \sqrt{2} \pi f N_1 \phi_m}$$




$(E_1 = 4.44 f \phi_m N_1)$ & Same for $(E_2 = 4.44 \phi_m f N_2)$

$$\left\{ \begin{array}{l} E_1 = 4.44 f B_m \cdot A N_1 \\ E_2 = 4.44 f B_m \cdot A N_2 \end{array} \right\}$$

[$\because \phi = B \cdot A$]

No-load operation:

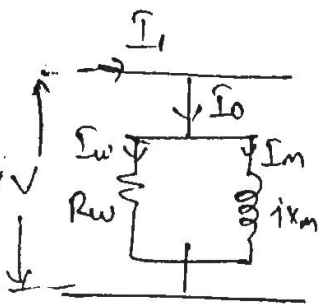


$I_0 \rightarrow$ No load current

$I_w \rightarrow$ wattful current / current (loss component)

$I_m \rightarrow$ magnetization current / current (Responsible for to set mag. flux)

$$\ast I_1 = I_0 = \underline{\underline{2 \text{ to } 5\% \text{ of } I_{f.L.}}$$

$$\vec{I}_0 = \vec{I}_w + \vec{I}_m$$

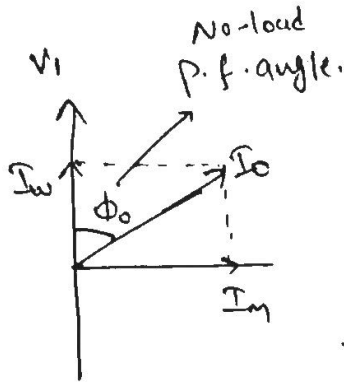


$$\rightarrow \left\{ \begin{array}{l} \phi_0 \rightarrow > 75^\circ \\ \& < 90^\circ \end{array} \right\}$$

\rightarrow No-load p.f. is very low $\rightarrow (0.2 \text{ or } 0.3)$

Ideal Transformer

$\rightarrow \infty$ Permeability of Core.

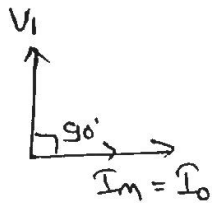It means negligible current is required to magnetize the circuit.



Note:

In ideal Xmer ϕ_0 will be 90° .
But in normal Xmer ($75^\circ - 90^\circ$).
(~~$75^\circ \phi < 90^\circ$~~)

IDEAL Transformer:

which has following properties:

- 1) Primary & Secondary winding resistances are negligible
- 2) Core has high Permeability (μ)
- 3) leakage flux & leakage Inductance are zero.
- 4) There are no losses due to resistance, hysteresis and eddy currents. ~~loss~~ and efficiency is 100%

Transformer ON No-load

* At No-load Primary winding is open-circuited.
& Primary current is zero.

* When an alternating voltage is applied to Primary, a small current I_0 flow in the Primary.

$I_0 \rightarrow$ is called no-load current of transformer.

It has two components I_m & I_w .

$\rightarrow I_m \Rightarrow$ is called magnetizing component, it magnetizes the core, it set up the flux in core & therefore I_m is in phase with Φ_m .
($I_m \rightarrow$ magnetizing component, also called reactive or wattless component of no-load current).

$\rightarrow I_w \Rightarrow I_w$ supplies the hysteresis & eddy current losses in the core & the negligible I^2R loss in the primary winding. I_w also called Active component or wattless component of no-load current. It is in the phase with the applied voltage V_1 . The no-load current I_0 is small of the order of 3 to 5% of rated current of primary.