

Electronics Measurement & Instrumentation

4EC3-06

Unit -2

Electronic Instruments

Dr. Girraj Sharma

Associate Professor

**Department of Electronics & Communication Engineering
JAIPUR ENGINEERING COLLEGE AND RESEARCH CENTRE, JAIPUR**

4EC3-06: Electronics Measurement & Instrumentation

Credit: 3

Max. Marks: 150(IA:30, ETE:120)

3L+0T+0P

End Term Exam: 3 Hours


ELECTRONIC INSTRUMENTS - Electronic Voltmeter, Electronic Multimeters, Digital Voltmeter and Component Measuring Instruments: Q meter, Vector Impedance meter, RF Power & Voltage Measurements, Introduction to shielding & grounding.

Electronic Voltmeter:

Electrical instruments



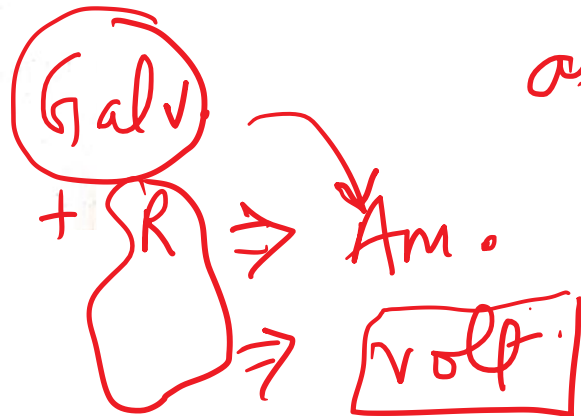- ① absolute insto give OP in form of write NO previous calibration or comparison is necessary.
 - ② secondary inst.
↓
OP determined from deflection of inst only when they have been calibrated by comparison from absolute insto
- eg. tangent galvanometer



abs. ins + comparison
+ calibration

in laboratories only

Basic principle:

- 1. Magnetic effect - for A & V
- 2. Electro dynamic " - for A & V
- 3. Electromagnetic " - wattmeter
- 4. Thermal - A & V.
- 5. Chemical - dc A-hr. meter
- 6. Electrostatic - V only

power → household meter

Secondary insto

① Indicating insto
Ordinary A, V & Watt meter

② recording insto
give a continuous record
using inked pen

③ Integrating insto
measure & register the total quantity of electricity
Amp-hr. & Watt-hr meter

electronic voltmeter

Essential of Indicating Instrument

- (i) Deflecting Torque :- utilize one or more factor from above
- (ii) Controlling Torque - [spring, gravity]
- (iii) Damping Torque ; to dec inertia

- ① moving iron type
- ② moving coil type
- ③ permanent magnet type
- ④ electrodynamic

Electronic Voltmeter; The voltmeter which uses the

amplifiers ~~for~~ ^{to} increases their sensitivity

→ It gives accurate reading because of high i/p Resistance

↳ detects signals of very weak strength

Digital voltmeter

~~Analog~~ Analog voltmeter

→ moving coil voltmeter is not able to detect low voltages

- Vacuum tube - measure current
- transistor or FETs - measure voltage only

↳ voltmeter

AC

FET
OP-Amp

Moving coil voltmeter; → The magnitude of measured voltage is directly proportional to the deflection of the pointer

- The pointer is fixed on calibrated scale
- The point at which the pointer deflects indicates the magnitude of i/p voltage


problem with moving coil voltmeter → Power

→ large problem is drawn from measured ckt because of which the error occurs in their reading.


μV

10⁶ V

→ amp → M

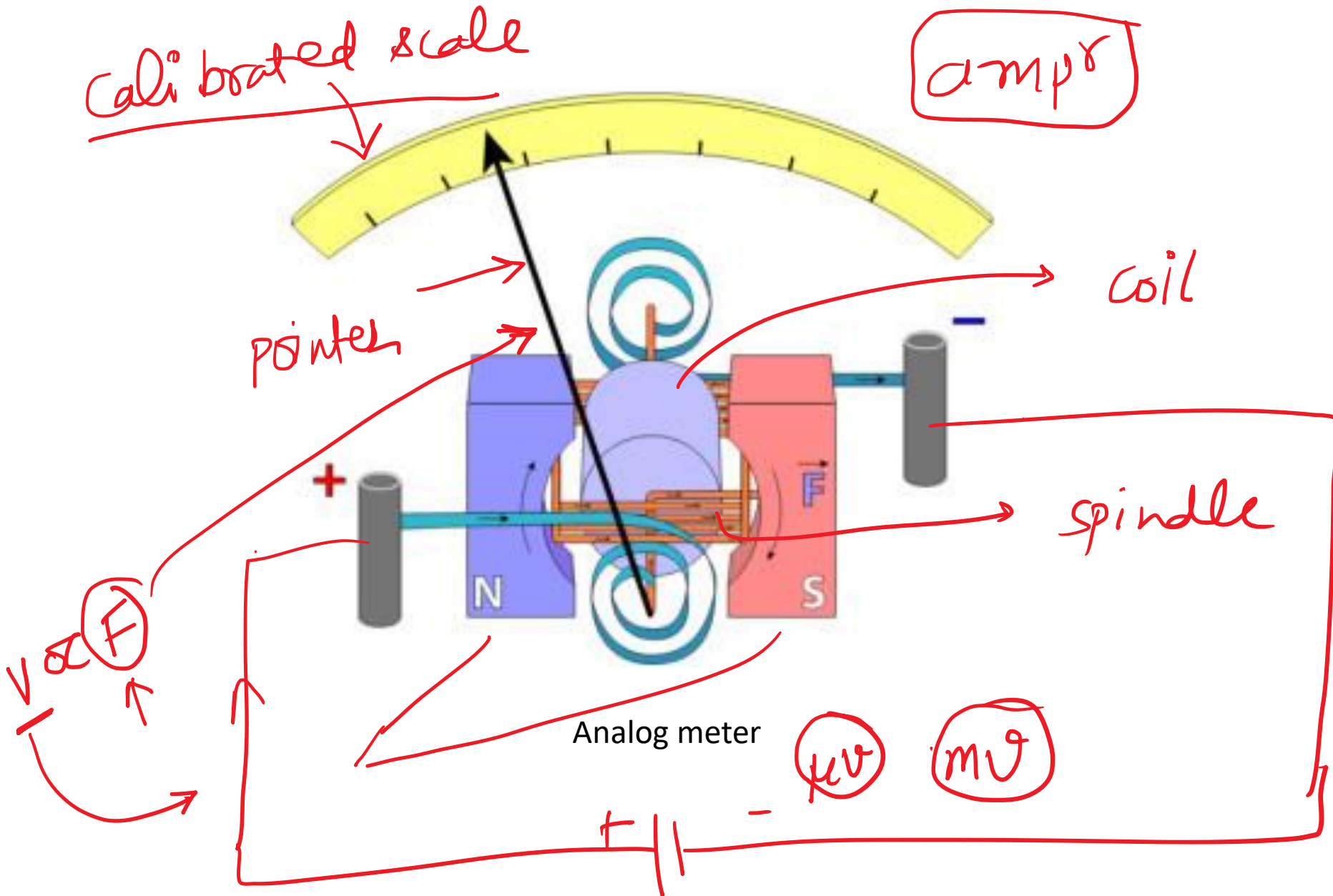


Electronic voltmeter

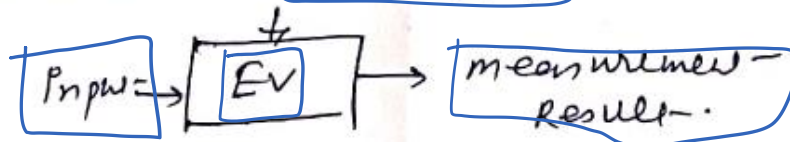

auxiliary amp's ckt

- In EV, the pointer is deflected by taking supply from auxiliary amplifier circuit.
- The extra power is not passing through the deflector, hence meter gives accurate reading.

def. of pointer

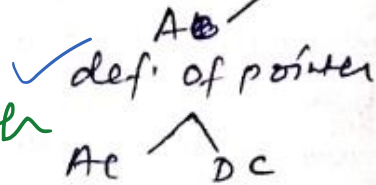

Dc ✓
gives digital o/p reading

→ seven segment

display / LCD
50mV / 50μV


Advantages of Electronic voltmeter;

- (1) Detection of low-level signals -
- ✓ (2) low power consumption
- (3) ✓ high freq range

T^r, FET's, Diodes

Basic electronic voltmeter (Transistor voltmeter) {DC}

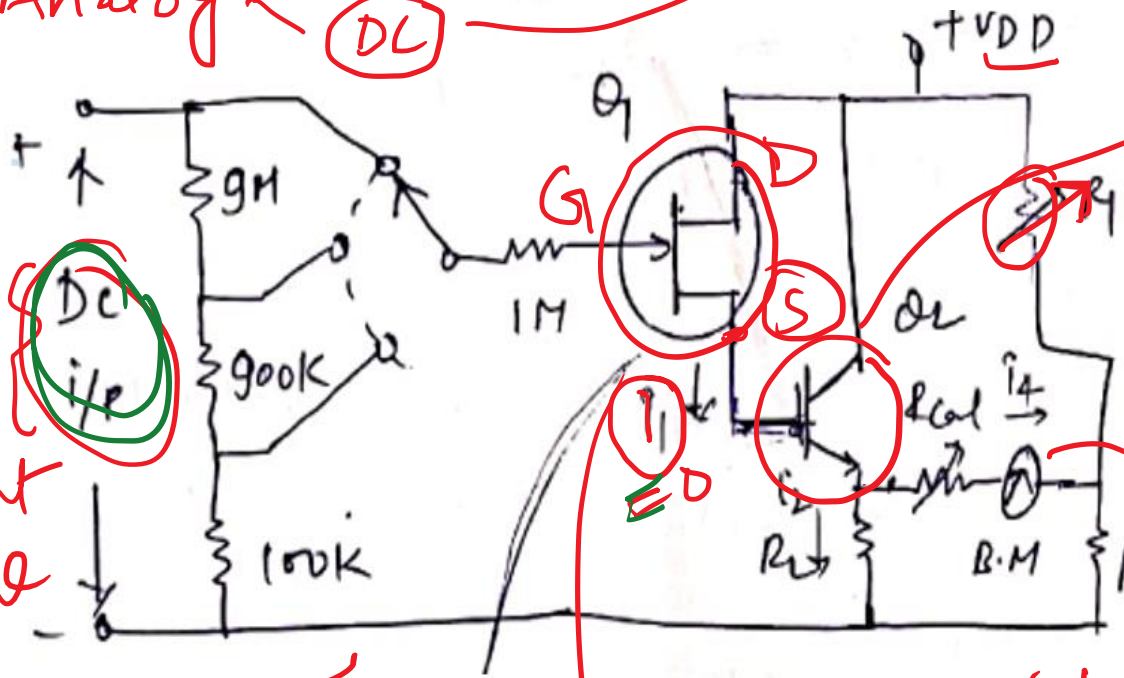↳ Analog $\left\{ \begin{matrix} AC \\ DC \end{matrix} \right.$



Input which we want measure

BJT

zero adjustment

Balanced CKT

meter

PMMC


0-2V
2-10V
10-100V

voltage divider

Range Selector

FET (source follower)
highest i_{in} i_{imp}
 $\frac{10V}{10} = 1A$

high sensitivity

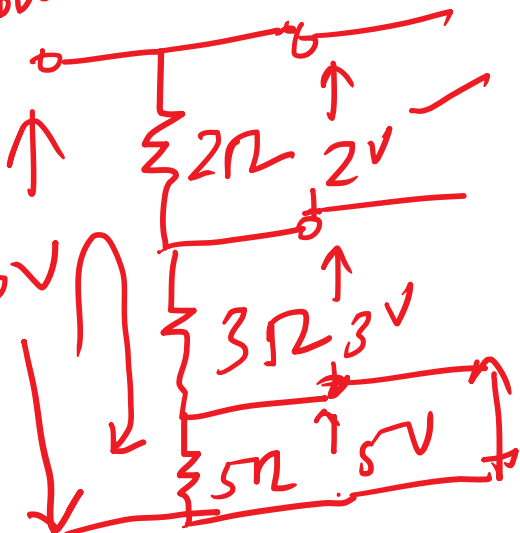

Input →


High I/P
I_{imp}

Meter

Moving coil

= 0

V_i

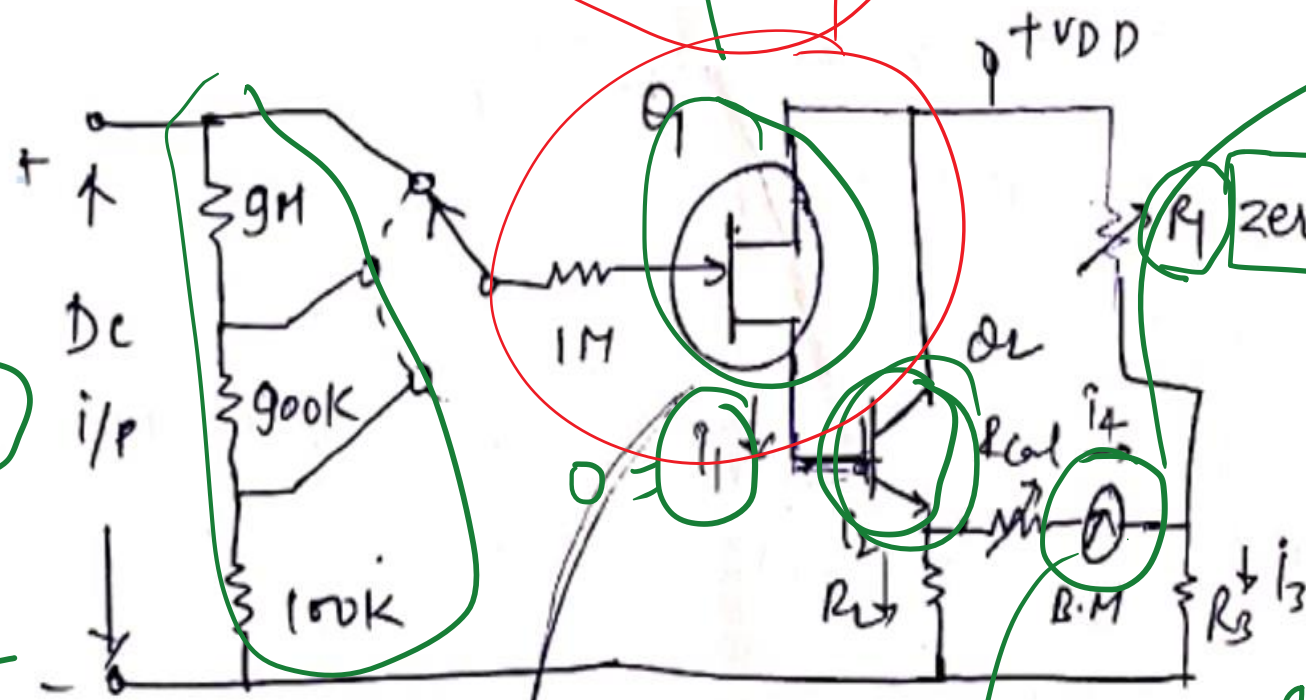

R₄ zero adjustment

$$i_2 = i_3$$

$$i_4 = 0$$

$i_2 \neq i_3$
 $i_4 \propto V_i$

Balancing condition

Reading = zero

- θ_2 with Resistor form balanced bridge ✓
- Bridge balance obtained by R_1 ✓
- zero I/P → meter show zero ✓
- bias on θ_2 is such $i_2 = i_3$ when I/P = zero ✓
- In this condition $i_f = 0$ ✓


- when I/P is applied bias on θ_2 incr ✓
- V_x incr ✓
- i_f flows through meter
- deflection of meter \propto I/P voltage


→ FET

- Advantage :
- (i) ✓ High I/P impedance to isolate meter from measurement ckt
 - (ii) Amount of power drawn is very low
 - (iii) Sensitivity very high (100 times the PMMC meter)
 - (iv) Can work in mV range
 - (v) overload can not damage the meter [Amp'r saturation & limit. current through meter]

② Differential voltmeter; (Analog/DC)

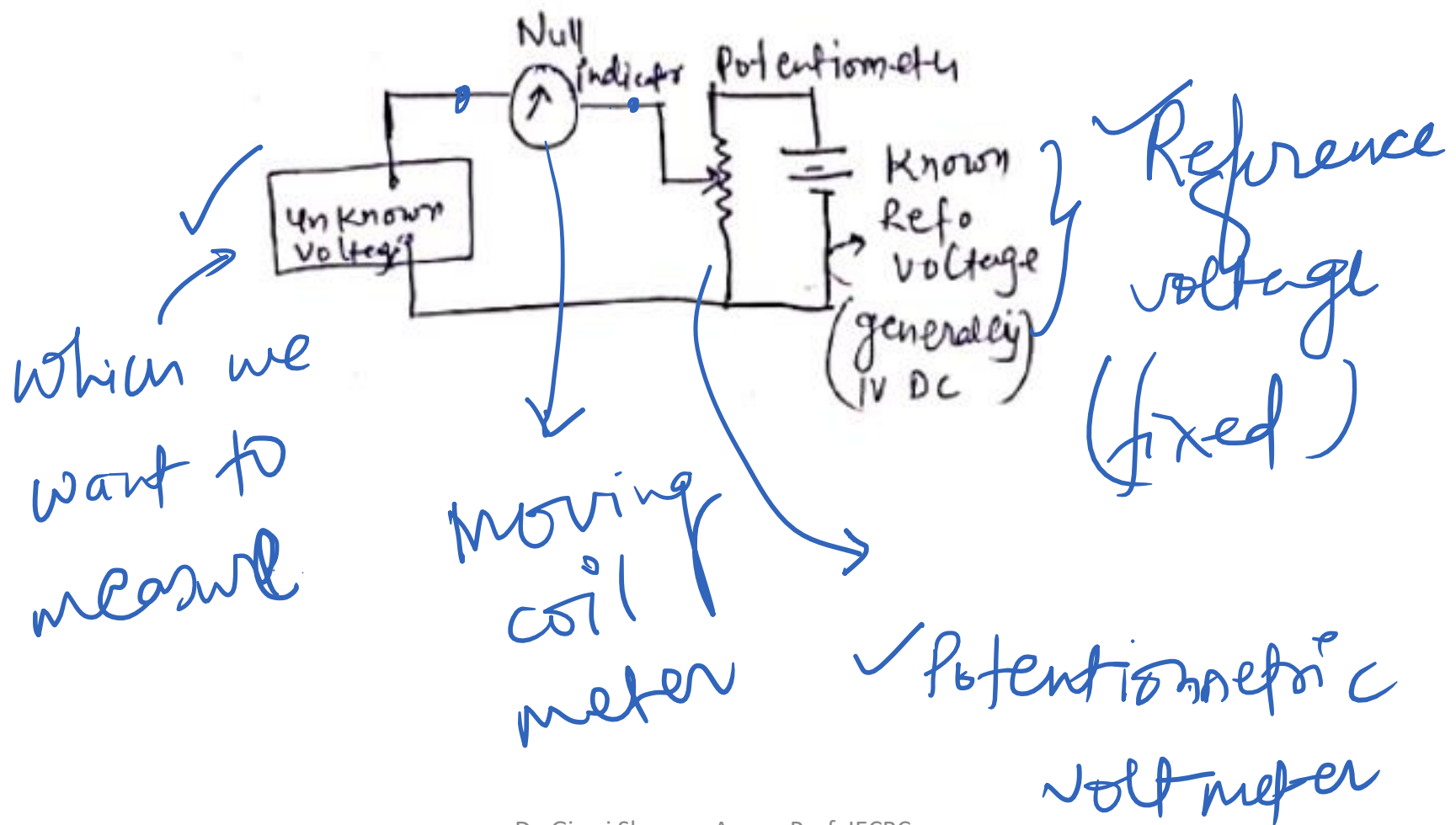→ It indicates difference B/w known & unknown voltages.
most common method of measuring unknown voltage.



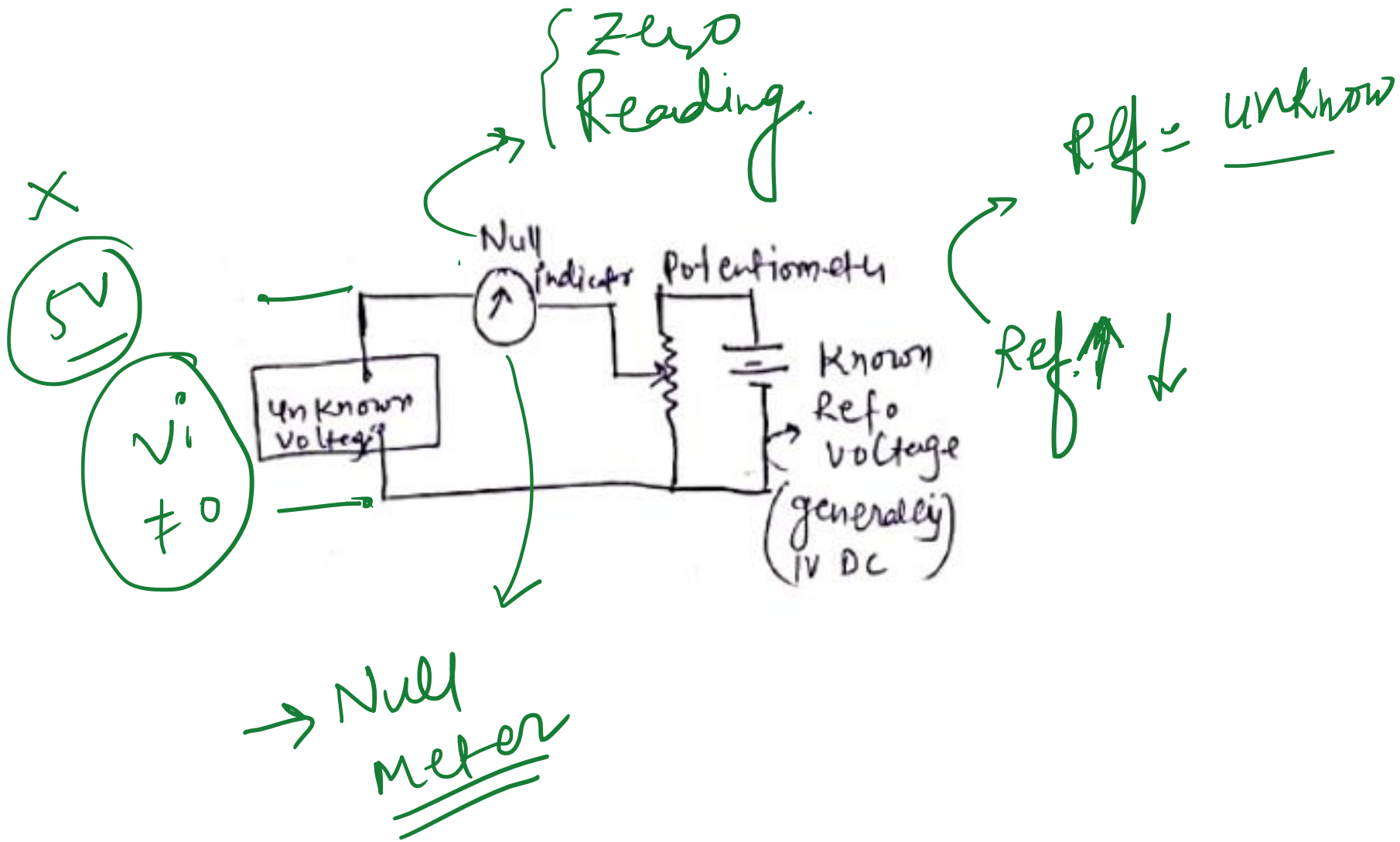

→ Principle similar to potentiometer hence also known as potentiometric voltmeter ✓


→ Pot. is varied till voltage across it becomes equal to unknown voltage

→ Equality is indicated by null detector

- When two voltages are same, two ends of null are at same pot. hence $i=0$
- $i=0$ indicates no impedance to unknown voltage
- Under null condition, voltage across divider is fraction of the known voltage & it can be measured which is nothing but unknown voltage

- ✓ Advantage - very high accuracy ✓
- ✓ high input impedance ✓

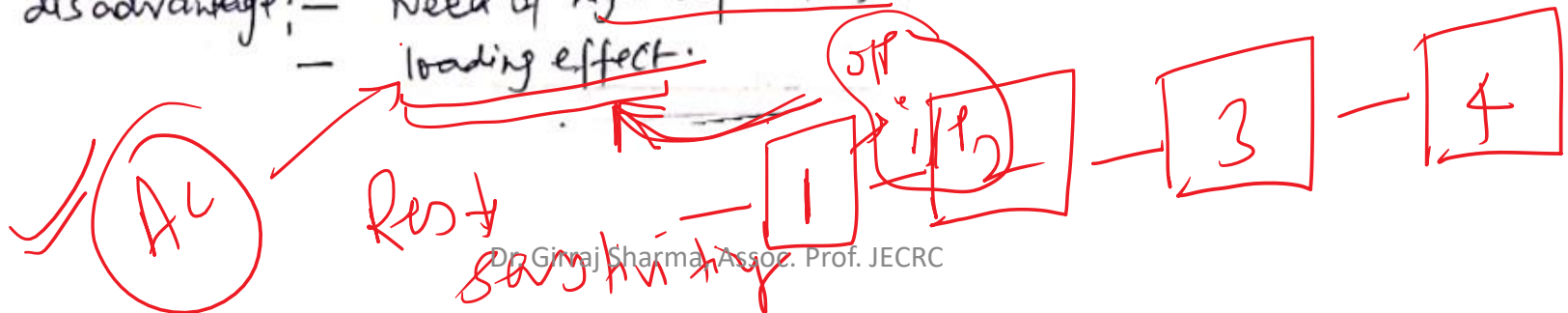
disadvantage: - Need of high ref. supply for high voltage measurement
- loading effect.



AC differential voltmeter

pure AC Amp ↑↑

DC diffⁿ voltmeter

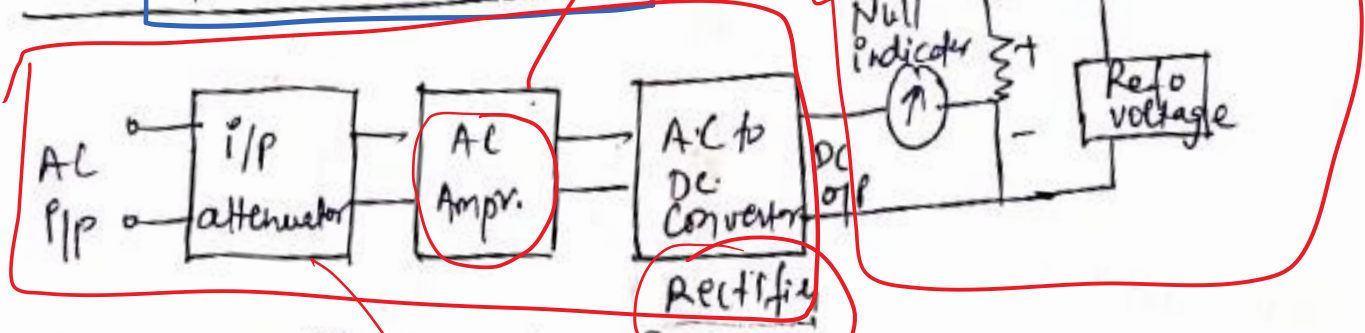

- AC is applied at the i/p
- AC applied to att. consisting no. of resistors used in voltage divider
- att. o/p → to ampr
- Ampr^r o/p → converted to DC using precision rectifier ckt.

~~AC + DC~~


AC → DC

i/p attenuator
↓↓ (dc)

AC

Average responding voltmeter:

AC / Analog voltmeter

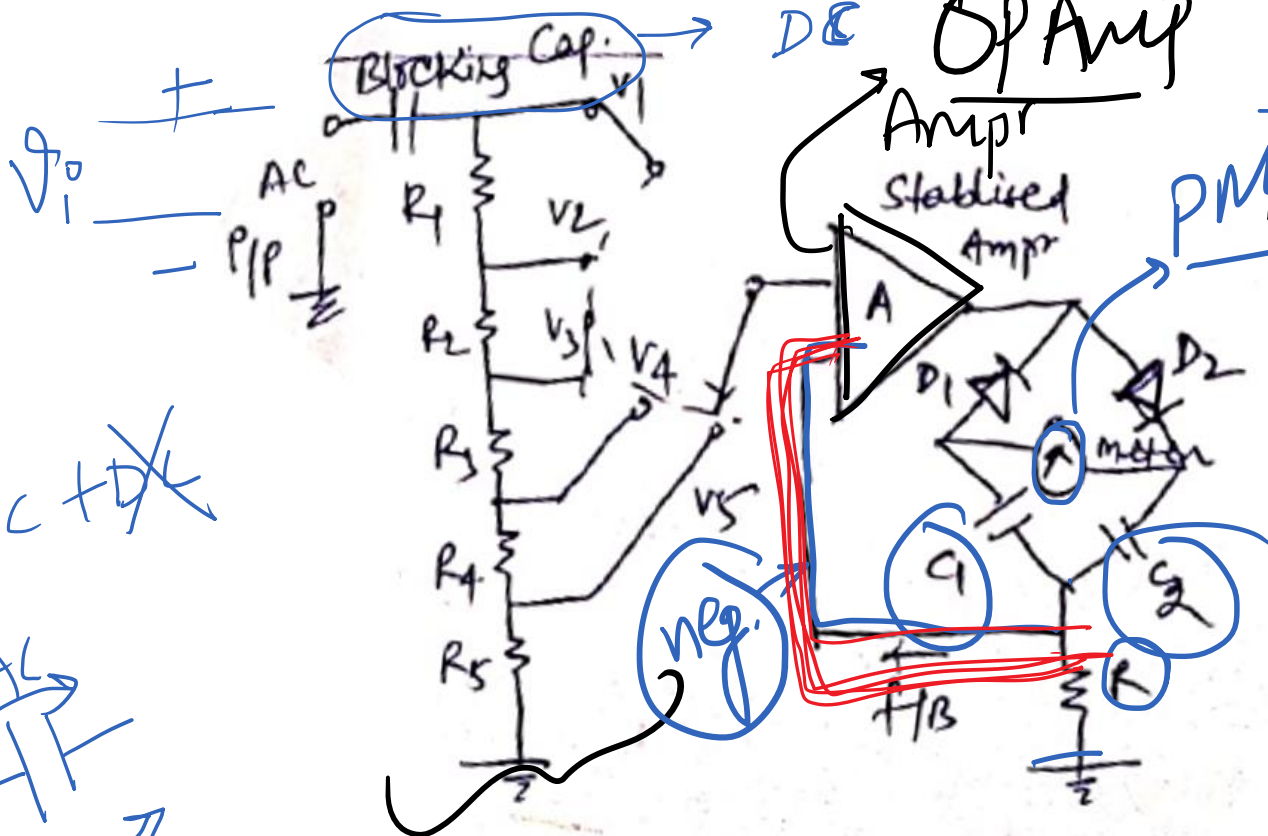

DC OPAMP

DC $\Rightarrow f=0$

AC $\Rightarrow f \uparrow$

$$X_C = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{\omega C}$$

DC \Rightarrow

$$X_C = \infty$$

~~AC + DC~~

AC \rightarrow
DC \rightarrow

Range selector

$$X_L = \omega L = 2\pi f L$$




ACT+DC

Dc

PMMC

Unknown voltage
AC
input
signal

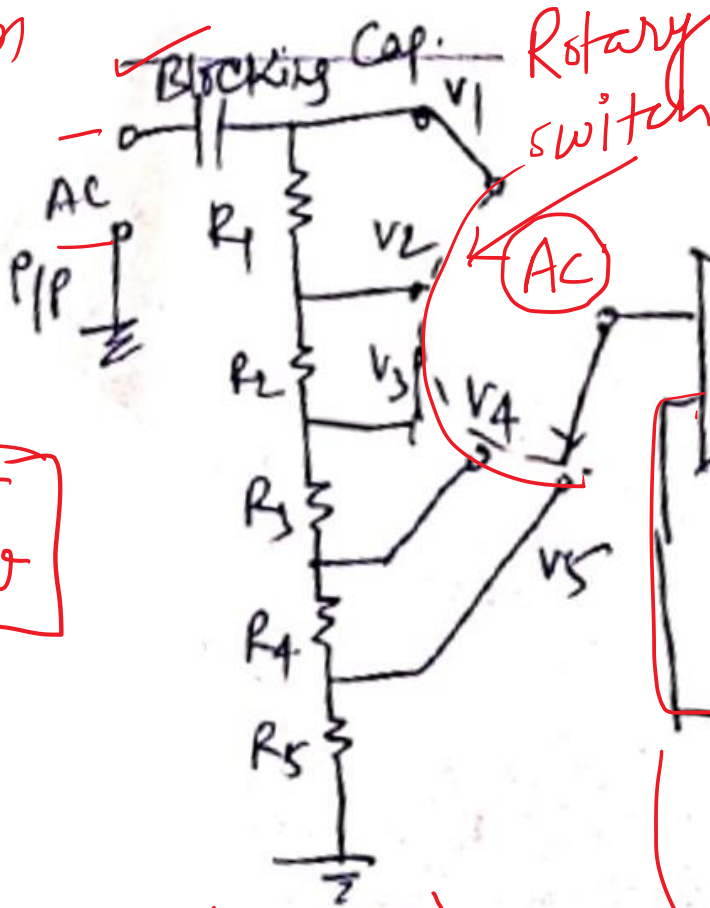


Stabilised Amp


Rectifying diode

AC → DC
Pulsating

filtering
Cap.

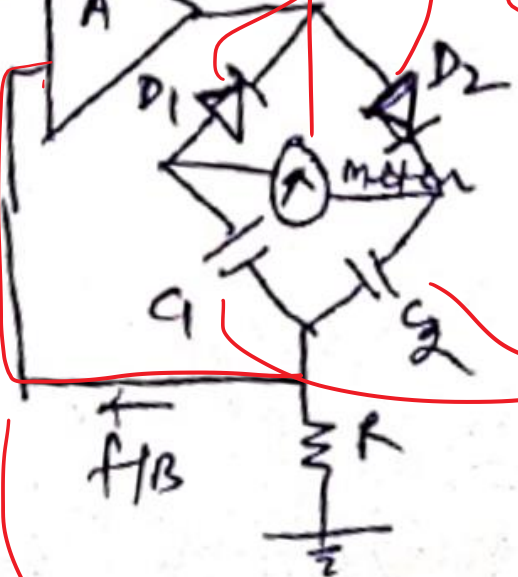

μV
 mV



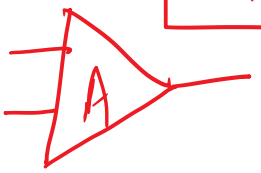


op-amp

→ + → OSC
→ -
Amp^r →


voltage divider
Range selector
stability

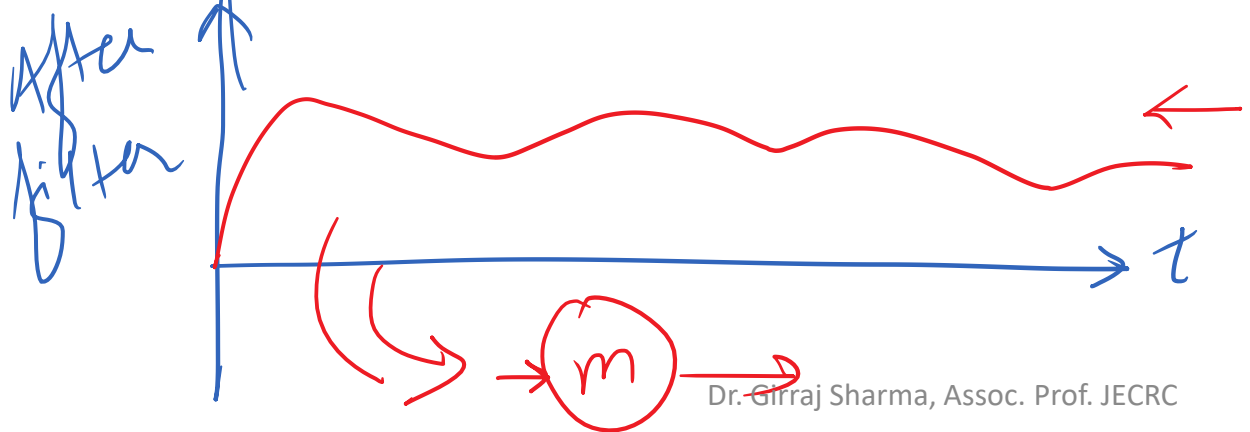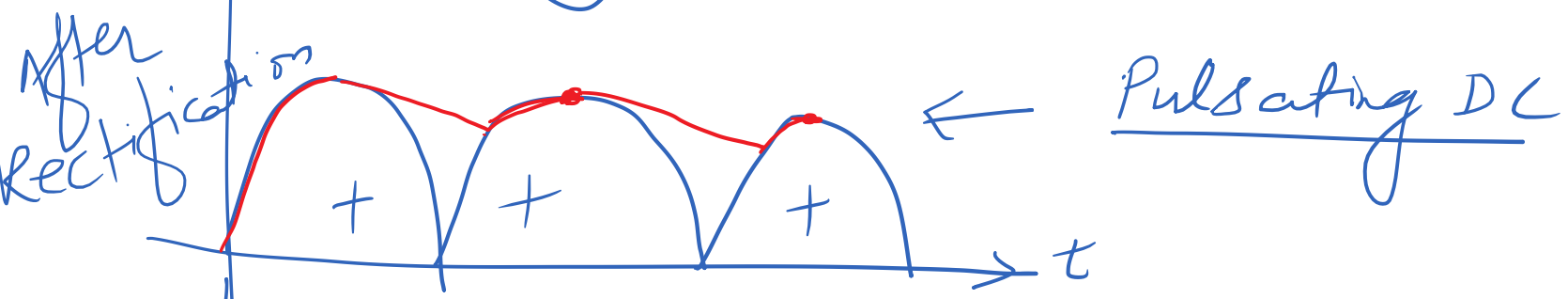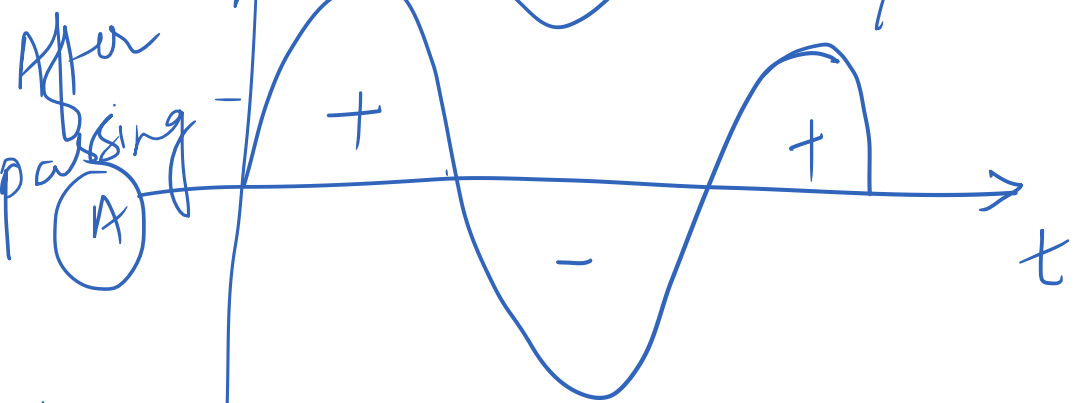- ① High I/P Impo
- ② Amp^r (input is low)



Average
i/p signal

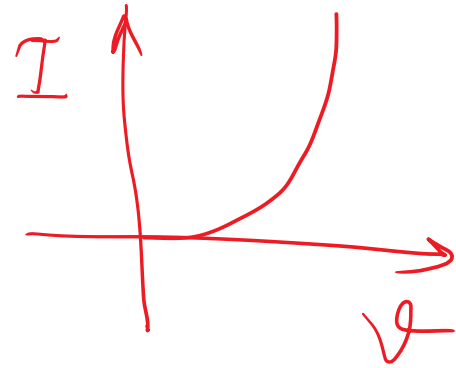- AC i/p amplified by A upon required level
- This voltage then rectified using D_1 & D_2
- rectified voltage fed to dc milliammeter
- Current obtain from rectifier is averaged by using a filter to produce steady deflection of meter pointer.



- blocking cap. used to blocks any dc compo in the i/p
- negative f/b is used to ensure stability for measurement
- Effect of diode nonlinearity is minimised by including meter in f/b
- C_1 & C_2 = storing cap. / filter cap. acts as coupling capacitor in f/b path
- rectified current is averaged using filter, the meter responds to avg.

reading of i/p

Advantages -

- diode non linearity minimised
- variation in meter impedance are compensated by negative feedback
- high freq range
- high i/p impedance

OP-amp

Disadvantage

- distorted, nonuniform, nonsinusoidal produce error in reading
- accuracy of meter depend on phase also.

FET voltmeter;

①

Difference Amplifier Type FET voltmeter

②

source follower type FET voltmeter

To incr i/p impedance


MOSFET

Transistor

FET
 Field effect Transistor
 high sensitivity

Analog / AC


Difference Amplifier Type FET voltmeter;

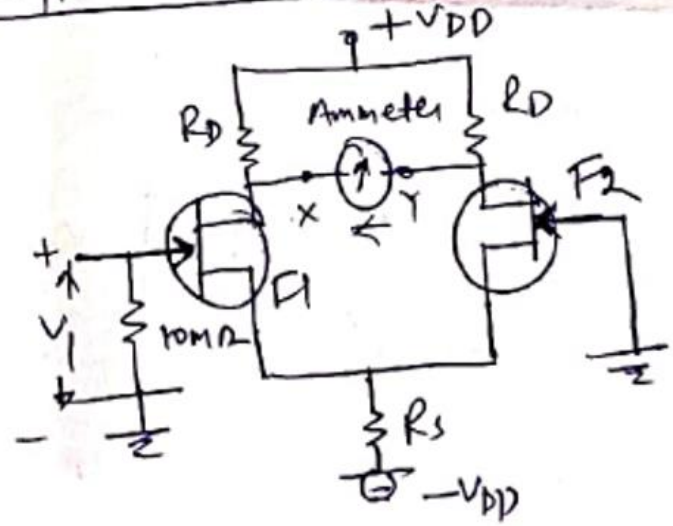

(differential ampr)

Bridge Type


FET voltmeter

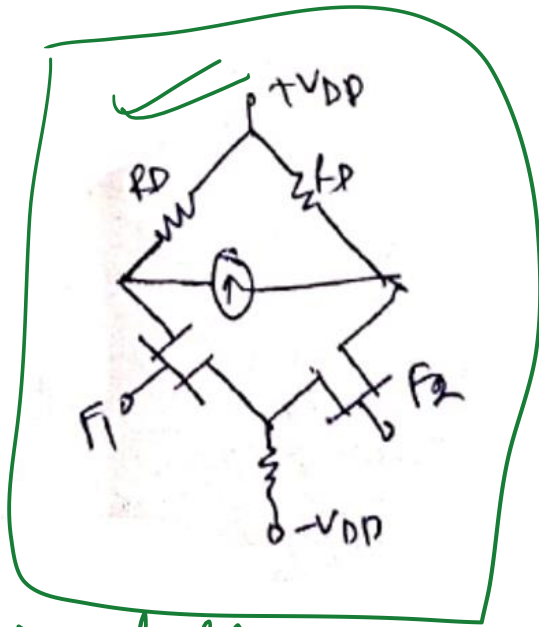

Difference Amplifier Type FET Voltmeter

(differential amp)

$P_{MVC} = \underline{\underline{zero}}$

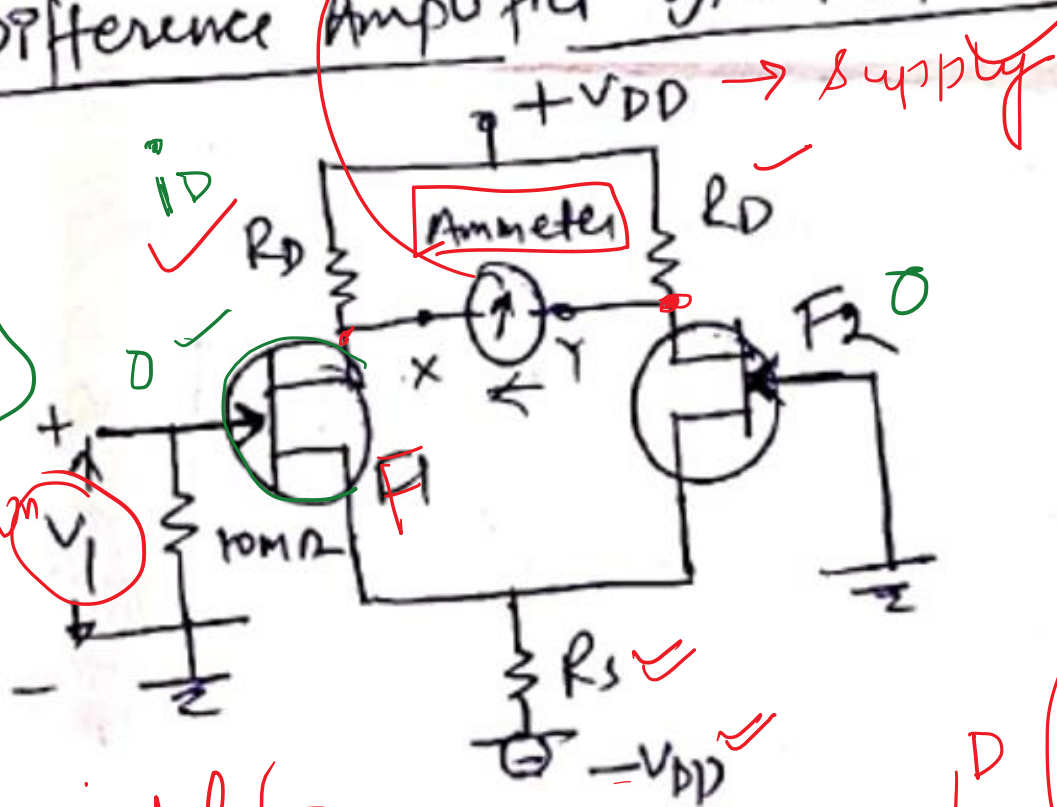

$V_1 = 0$

Unknown

Differential form

unknown voltage

Current in the meter



F_1, F_2 are two identical FET

same char

BJT \rightarrow E, B, C

BJT vs. FET ✓

→ F_1 & F_2 two FETs have matching char

req^r for thermal stability.


→ An incr in source current in one FET is offset by corresponding decr in ~~the~~ source current of other FET.

- ✓ R_D - upper arm of balanced bridge
- ✓ $F_1 F_2$ - lower arm

- Bridge is balance for two identical FET
Zero i/p produce zero current through predicting ammeter

- when neg. dc applied to gate of F_1 current will flow through ammeter

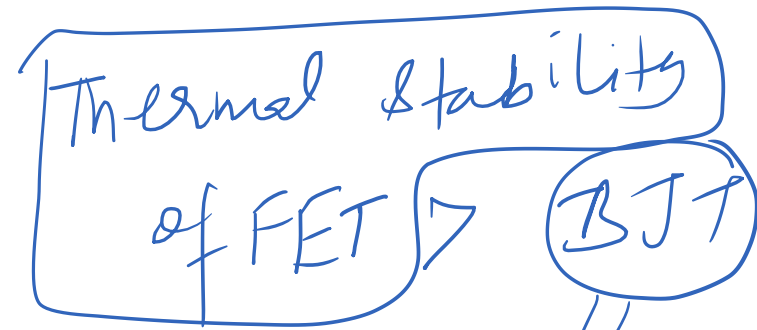→ magnitude of this current is proportion to input voltage



Thermal runaway

Parallel error

PMM

fast

seven seg LED

0 0

9 9

Digital voltmeter:

ADC

0, 1

binary, octal


0, 9

Converts the analog signals into digital & display the Hex voltages to be measured as discrete numericals instead of pointer deflection.


- Advantages -
- (i) less human reading errors
 - (ii) wide range (1V to 1000V)
 - (iii) highly accurate ($\pm 0.005\%$ of reading)

- (iv) better resolution (1 μ V) 10^{-6} V \rightarrow pointer
- (v) High i/p impedance (≈ 10 M Ω) \rightarrow incr sensitivity

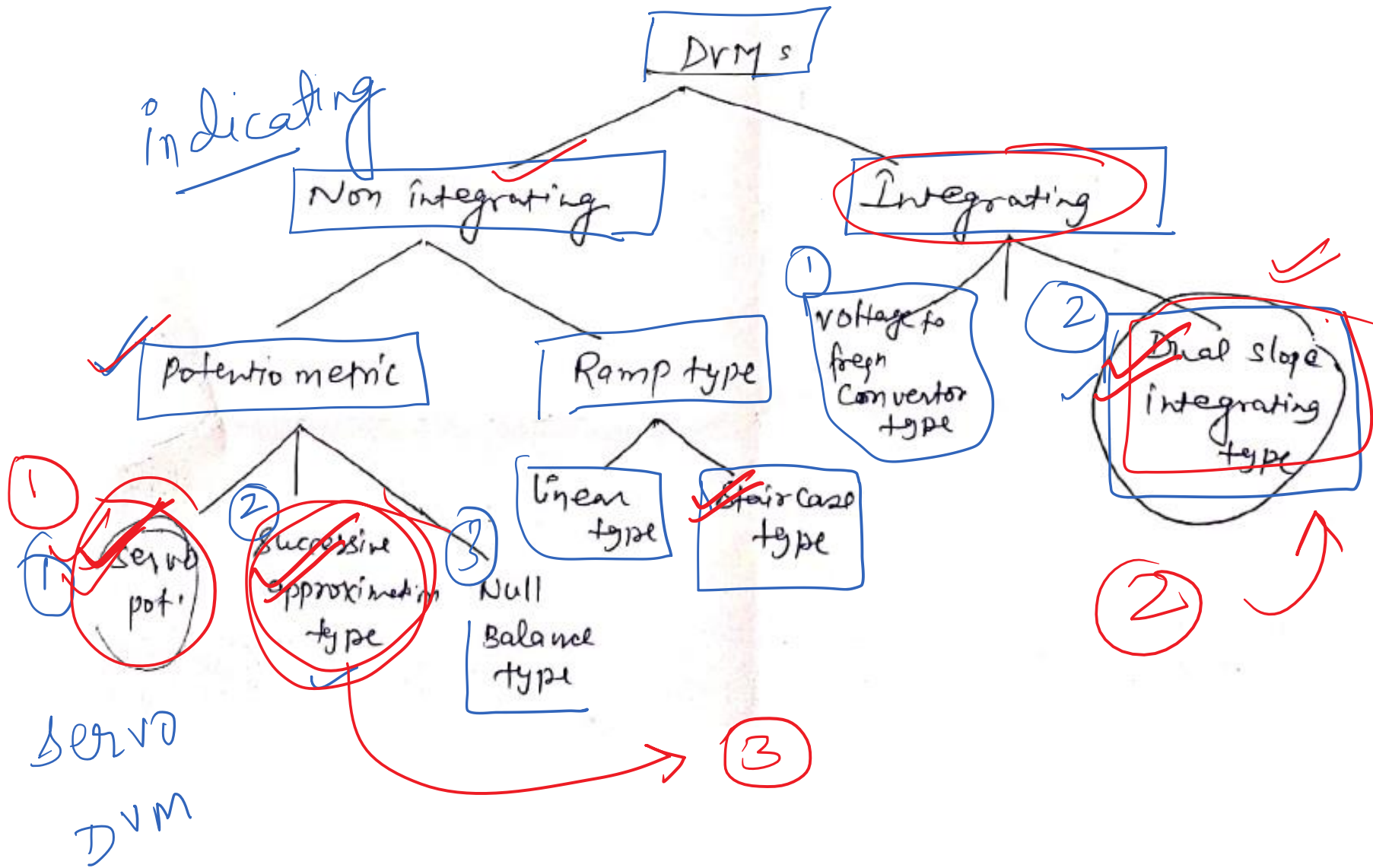- (vi) High reading speed.
- (vii) Can be programmed & computerised control.
- (viii) with development of IC chips, cost of DVM's is low
- (ix) portable (small size)
- (x) Internal calibration not dependent on measuring Ckt.
- (xi) BCD op can be printed or used for DSP
- (xii) Addition Ckt can be installed to measure, pressure, current, impedance, cap. etc




General Block diagram of DVM:-

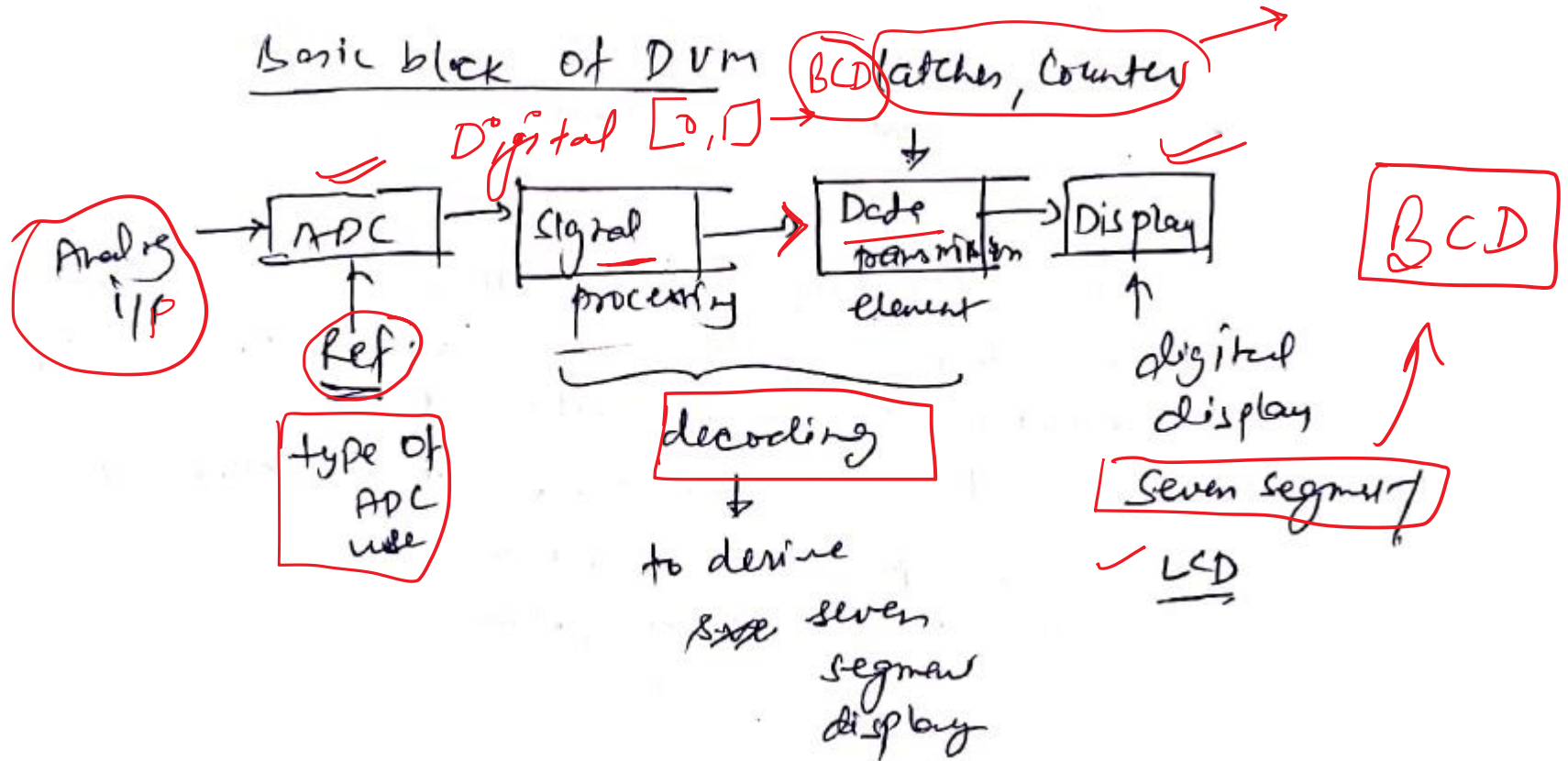


Servo potentiometric Type DVM;


Analog
voltage

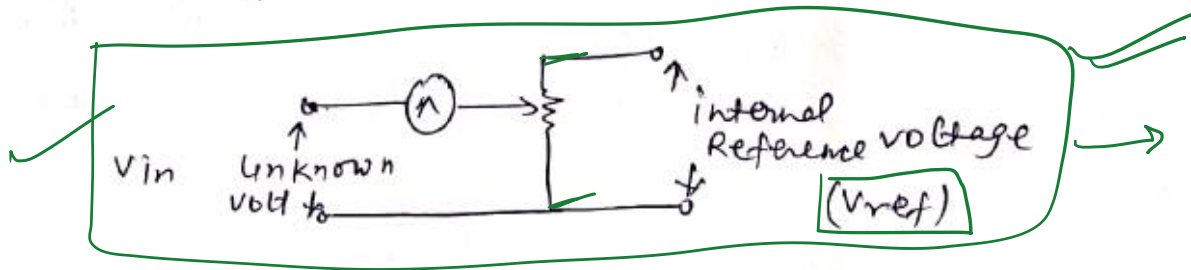

→ voltage comparison tech. is used to measure i/p voltage

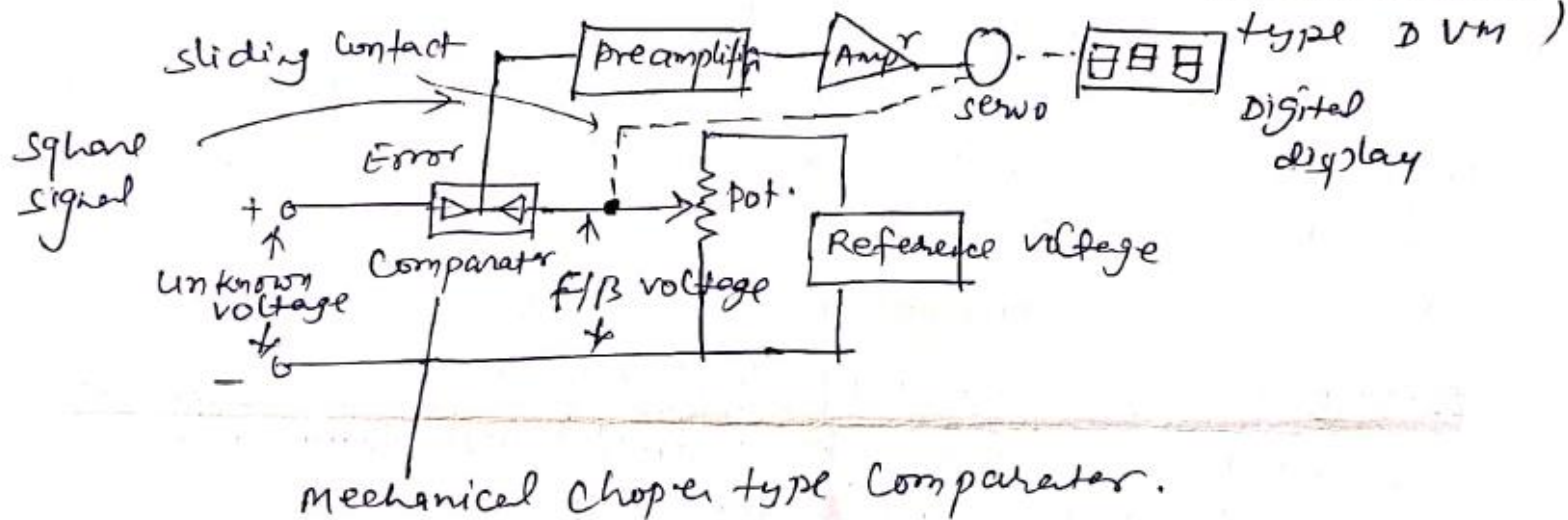
In DVM; null balancing is obtained automatically using a servomotor. this is called as (self balancing potentiometric



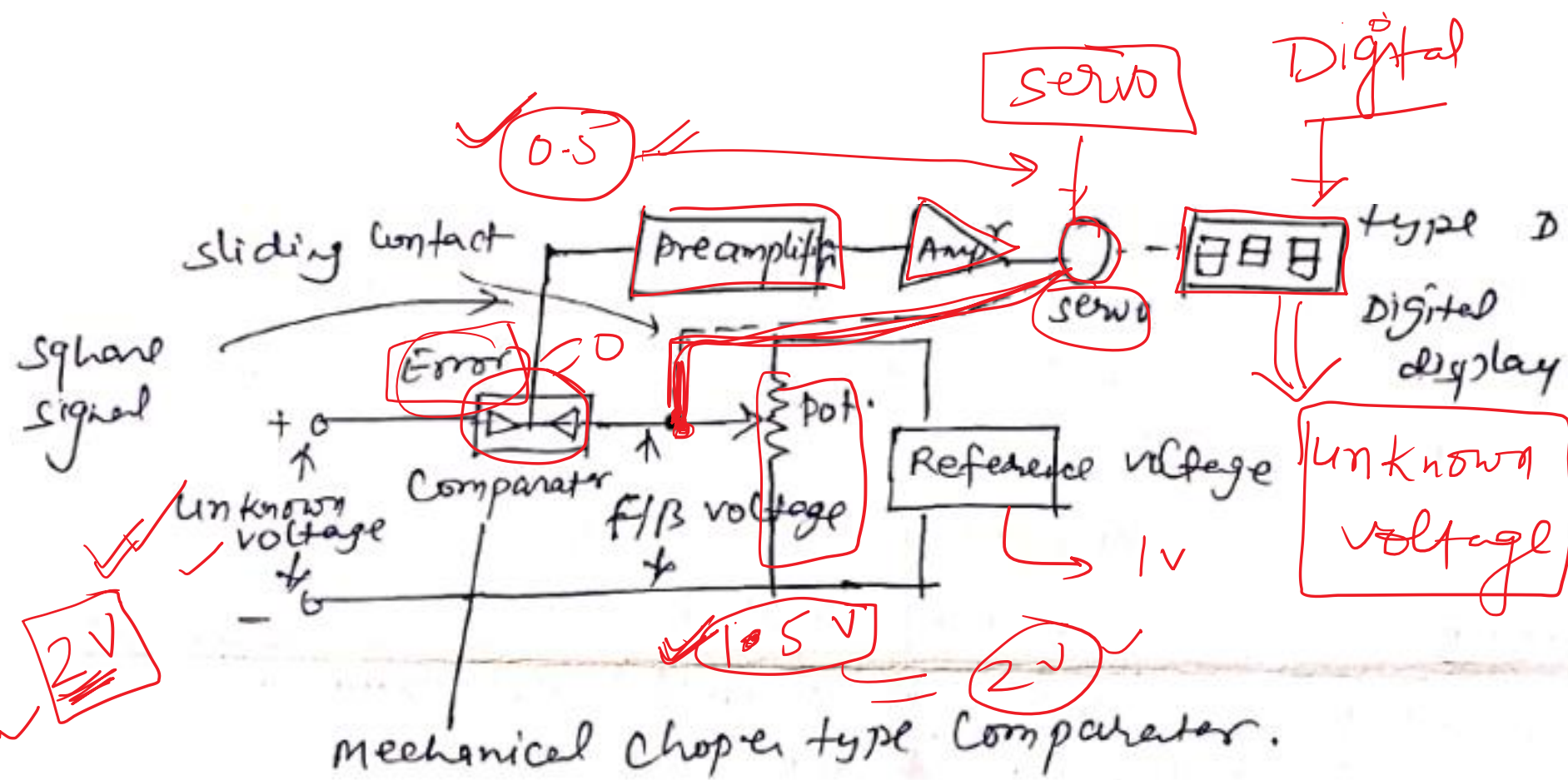


Mechanical chopper type Comparator.


dual slope integrating DVM

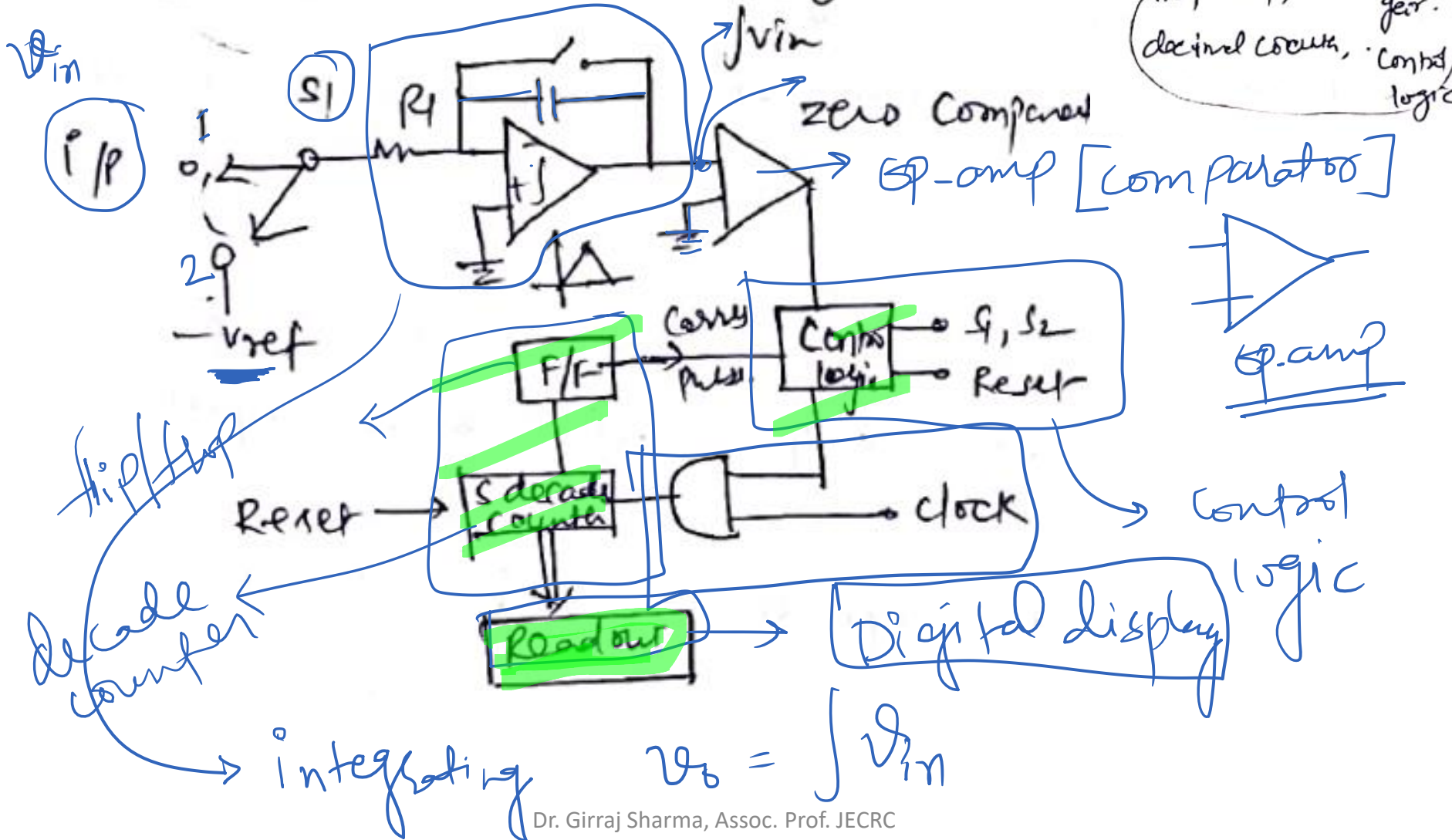

$\int c dt = ct$

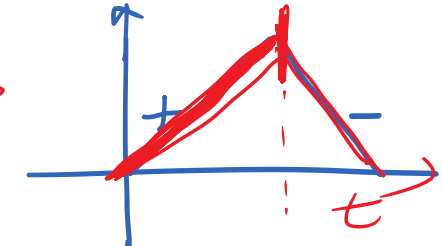

dual slope integrating DVM

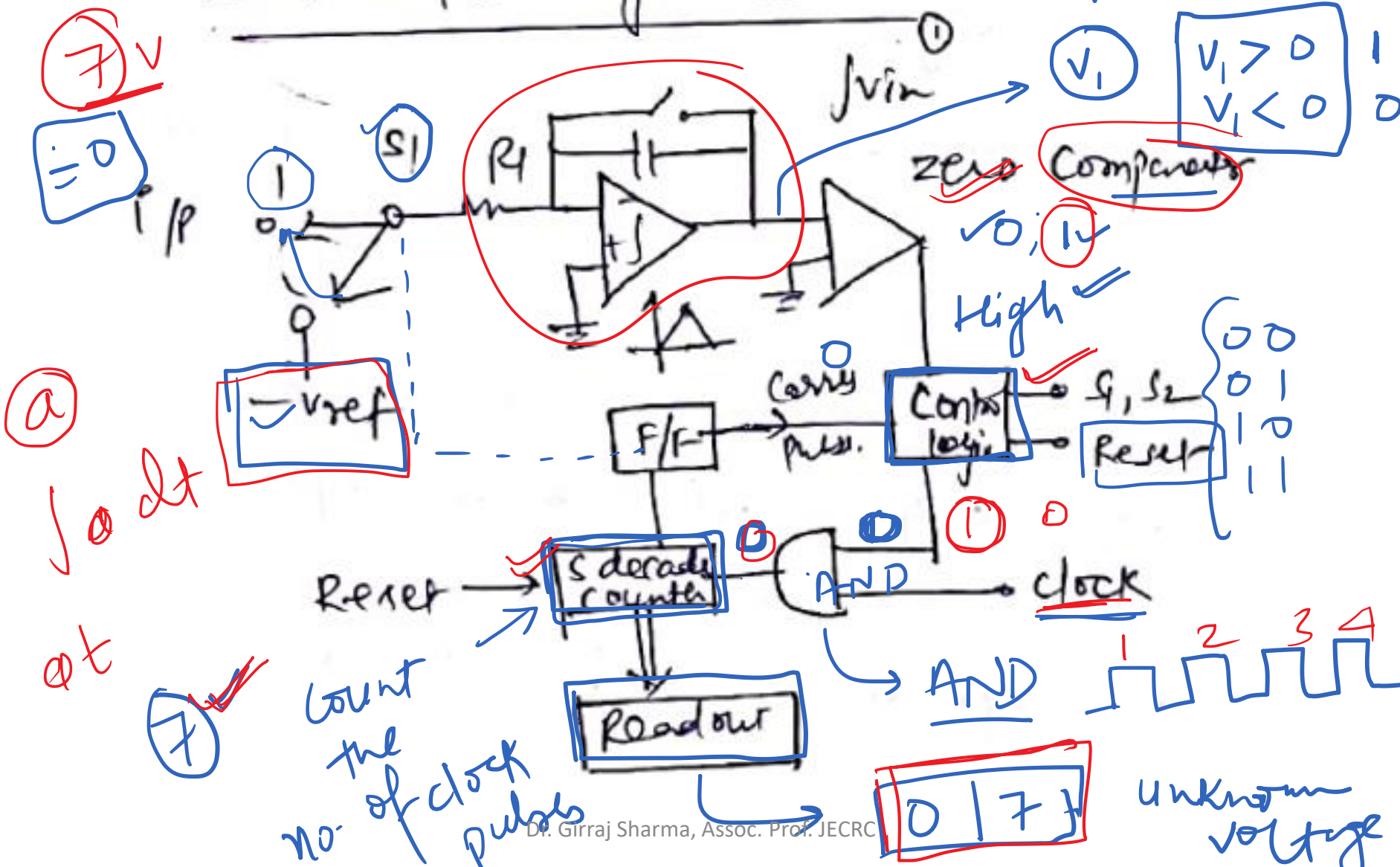

Step ① Counter reset to zero

OP of FF = zero

given to control logic

Control logic sends

to put S_1 at ①

integration starts
till t_1

→ Zero comparator OP changes

→ signal to Control logic which
opens the gate &
counting of clock pulse
starts

$$\text{Case ① } S_1 - \frac{V_{in} t_1}{R_1 C} = V_{01}$$
$$S_{ref} - \frac{V_{ref} t_2}{R_1 C} = V_{02}$$


Counter counts pulse & when reaches 9999 it generates
a carry flag pulse and all 8 digits go to zero.

FF OP → activated to logic level 1

This activates the control logic. This sends

a signal which change S_1 position ② → $-V_{ref}$ connect to int. → Reverse
Cap discharge.

Successive Approximation Type DVM

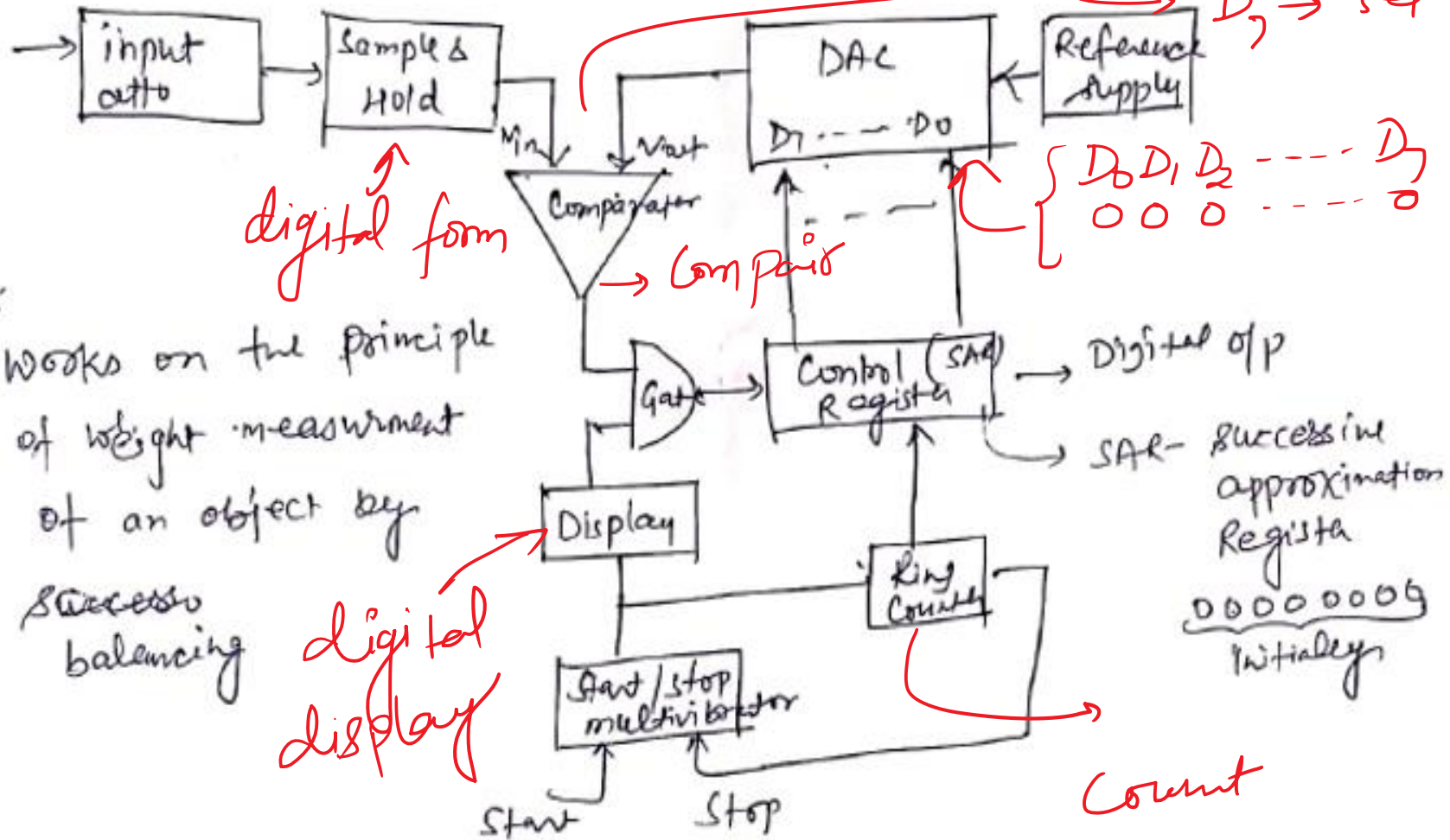


Works on the principle of weight measurement of an object by successive balancing


V_{in}	Operation	V_{out}								Compare	Comparator output	Action
		D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0			
00110011	D_7 Set	1	0	0	0	0	0	0	0	$V_{in} < V_{out}$	-Ve	D_7 Reset
00110011	D_6 Set	0	1	0	0	0	0	0	0	$V_{in} < V_{out}$	-Ve	D_6 Reset
00110011	D_5 Set	0	0	1	0	0	0	0	0	$V_{in} > V_{out}$	+Ve	D_5 Set
00110011	D_4 Set	0	0	1	1	0	0	0	0	$V_{in} > V_{out}$	+Ve	D_4 Set
00110011	D_3 Set	0	0	1	1	1	0	0	0	$V_{in} < V_{out}$	-Ve	D_3 Reset
00110011	D_2 Set	0	0	1	1	0	1	0	0	$V_{in} < V_{out}$	-Ve	D_2 Reset
00110011	D_1 Set	0	0	1	1	0	0	1	0	$V_{in} > V_{out}$	+Ve	D_1 Set
00110011	D_0 Set	0	0	1	1	0	0	1	0	$V_{in} > V_{out}$	+Ve	D_0 Set

Amp Type DVM

input

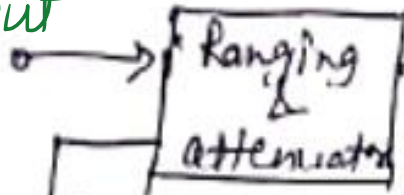






Select a Range

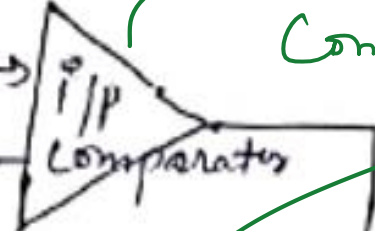

OP amp comparator Comp 1




Start pulse {Enable} digital display

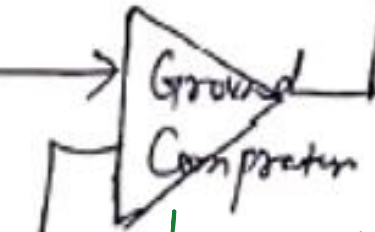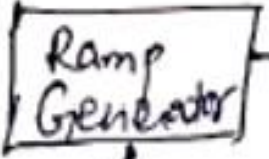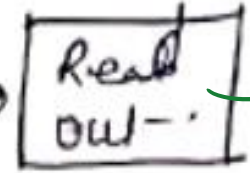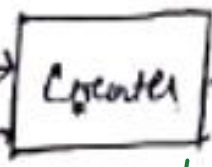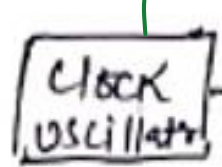


Comp 2

Stop pulse

Count the clock pulses

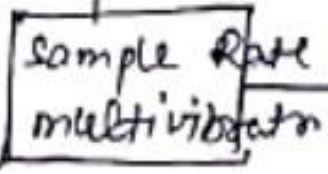


Negative going Ramp signal is generated

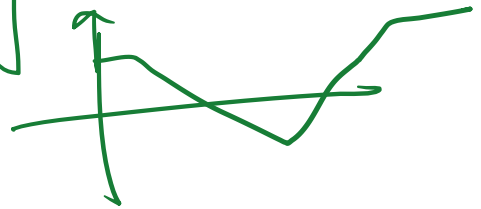

→ Based on voltage to time conversion technique.

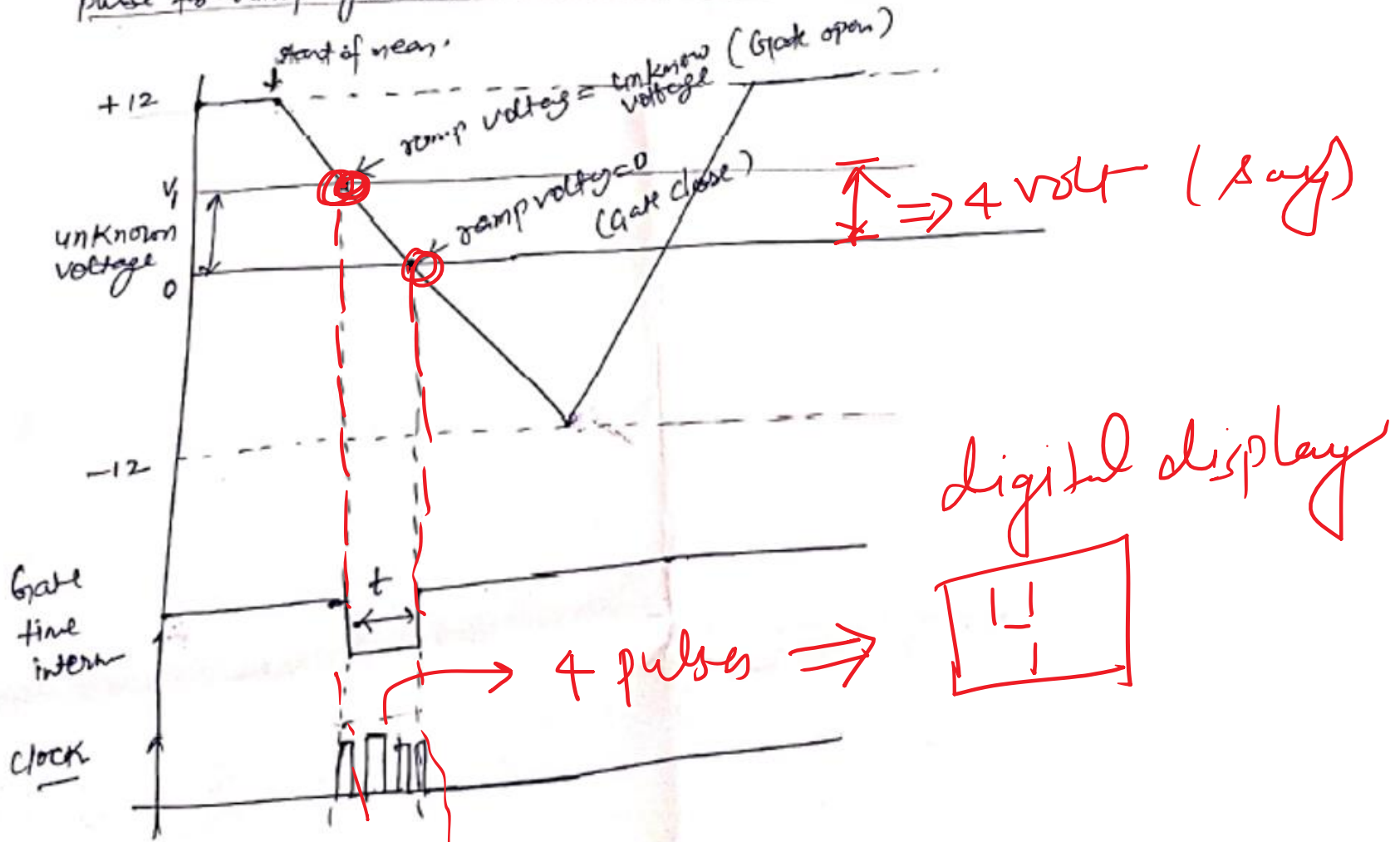→ The sample rate multivibrator determines the rate at which the measurements cycles are initiated & also provides initiating pulse for ramp generator to start its next ramp voltage.



Digital multi meter:

→ Capable of measuring ac voltages, dc voltages, ac and dc currents and resistances over several ranges.

Voltage $\begin{cases} AC \\ DC \end{cases}$


Current $\begin{cases} AC \\ DC \end{cases}$

Resistance

① AC → DC → Digital → Digital

② $V \rightarrow I \rightarrow$

③ $R \rightarrow V = IR$

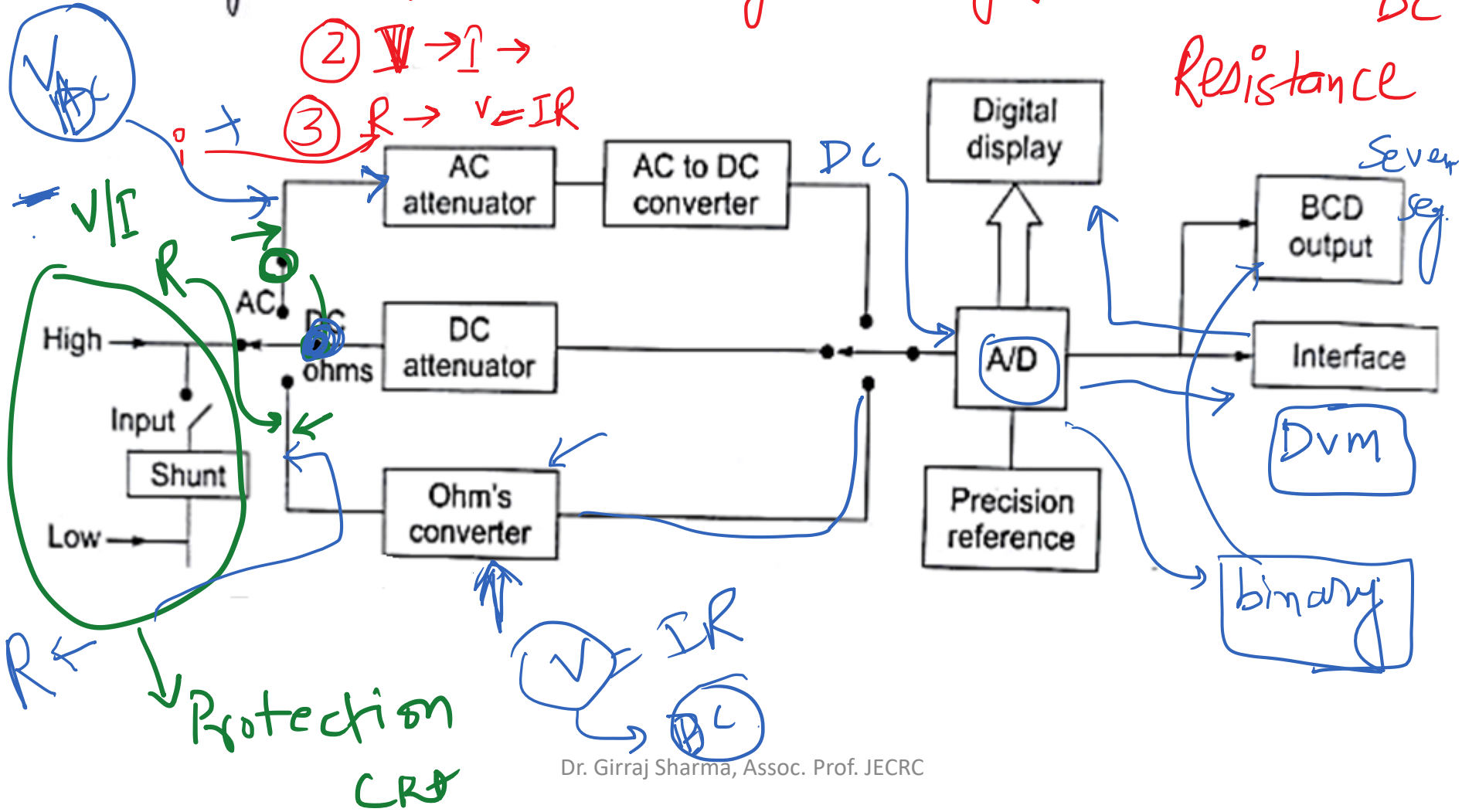

~~DCV~~
DCV

BC107

NPN/PNP
T_h



0-2K

(+)

(-)

DCA

hfe gain of T_h

V/Ω/mA (+)

COM (-)

- Current is converted to voltage by passing through low shunt resistance
- A.C quantities are converted to dc. by using rectifiers
- All quantities are digitised using A/D converter & displayed in digital form on the display


→ Advantages

- ↳ low price, small size, immune from electric noise
- ↳ can be used with external equipment

 used to measure freqⁿ

Digital Freqn meter ;


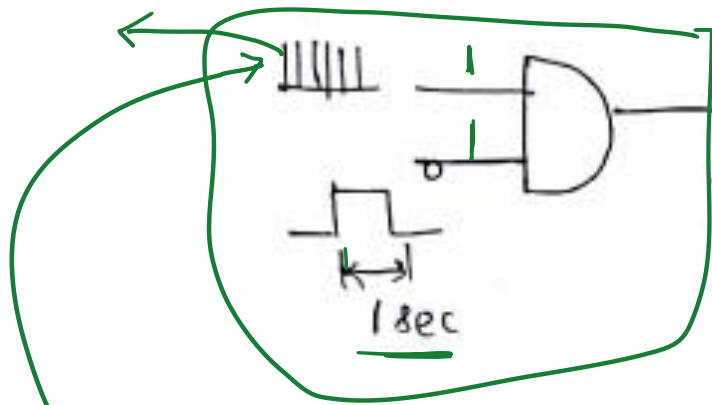
Signal → trigger pulses $f = \frac{N}{t}$
 1 sec



1 sec
 no. of pulses counted = freqn.

T^o 555

→ NAND

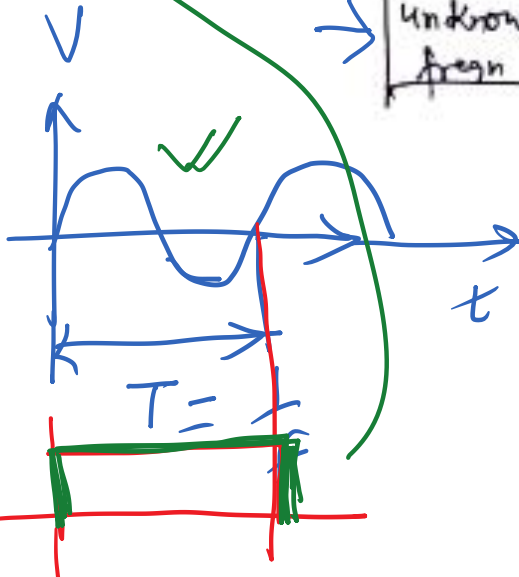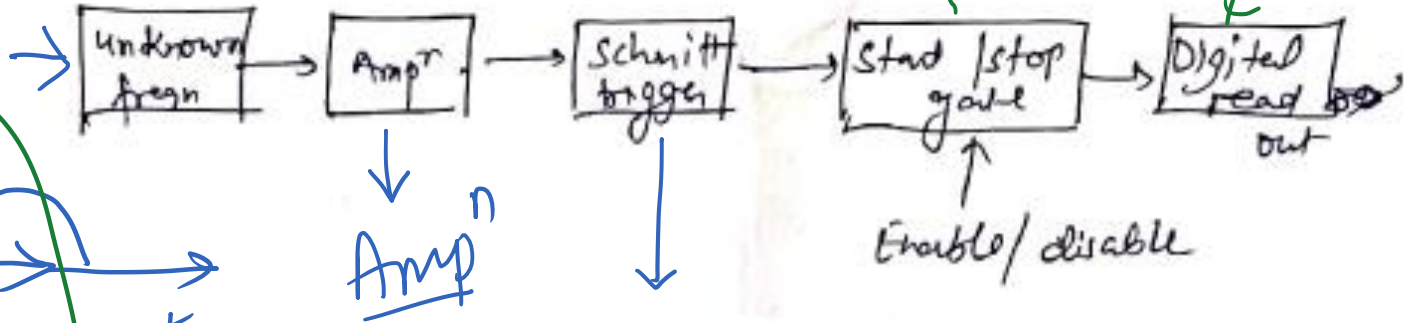

Analog signal → square signal
 (sinusoidal)

Imp.

Q-meter:

↳ Device used for testing radio freq coils (RFC), inductors and capacitors.

$$Q = \frac{\omega_0 L}{R}$$

Q-meter is an instrument which is designed to measure the value of Q; directly & very useful in measuring characteristics of coils and capacitors.


Q - storage factor

ω_0 = resonant angular freq

L = inductance

R = effective resistance of coil

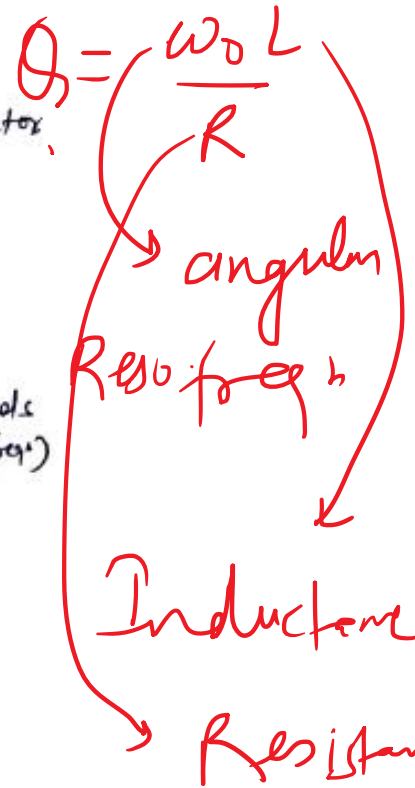↳ never determined directly (depends on freq)



Working principle:

↳ series resonant ckt

at resonant freq f_0

$$X_C = X_L$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$$\text{current } I_0 = \frac{E}{R}$$

$$\text{voltage across cap. } E_C = I_0 X_C = I_0 X_L = I_0 \omega_0 L$$

$$\text{input voltage } E = I_0 R \therefore \frac{E_C}{E} = \frac{I_0 \omega_0 L}{I_0 R} = \frac{\omega_0 L}{R} = \underline{Q}$$


$$\boxed{E_C = Q E}$$

input is ^{cap} magnified Q-times.

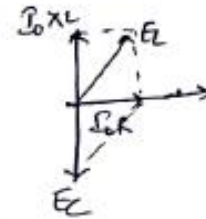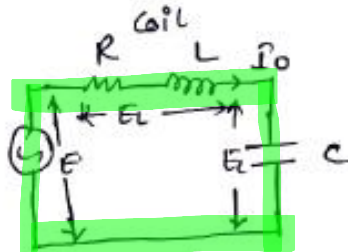

Working Principal of Q-meter :

Series Resonant Ckt :

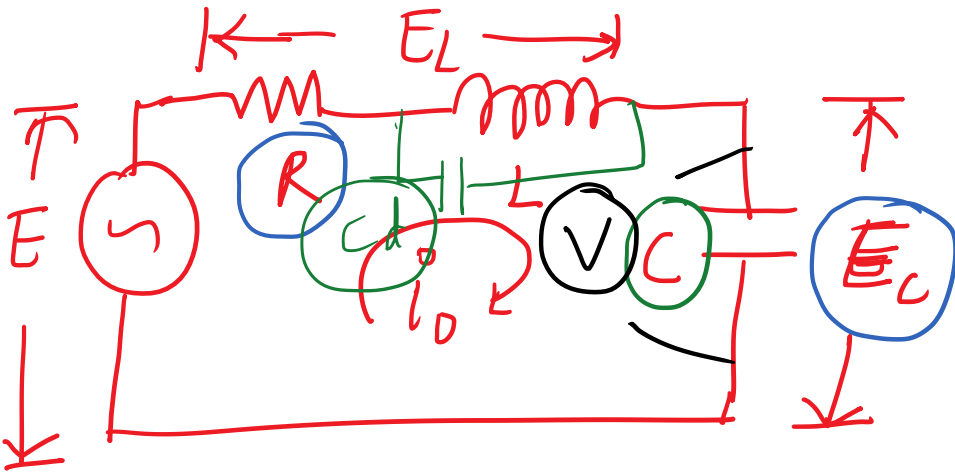

at Resonance

$$X_C = X_L$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$X_C = \frac{1}{\omega_0 C} \quad X_L = \omega_0 L$$

$$I_0 = \frac{E}{R}$$

$$Q = \frac{E_C}{E}$$

$$E_C = I_0 X_C = I_0 X_L$$


$$E_C = I_0 \omega_0 L$$

$$E_C = Q E$$

$$E_C = E \left(\frac{\omega_0 L}{R} \right) \rightarrow Q$$

If r.p.p voltage is kept const; the voltage appearing across the capacitor is Q times E and a voltmeter connected across the cap. can be calibrated to read the value of Q directly.

Practical ckt;

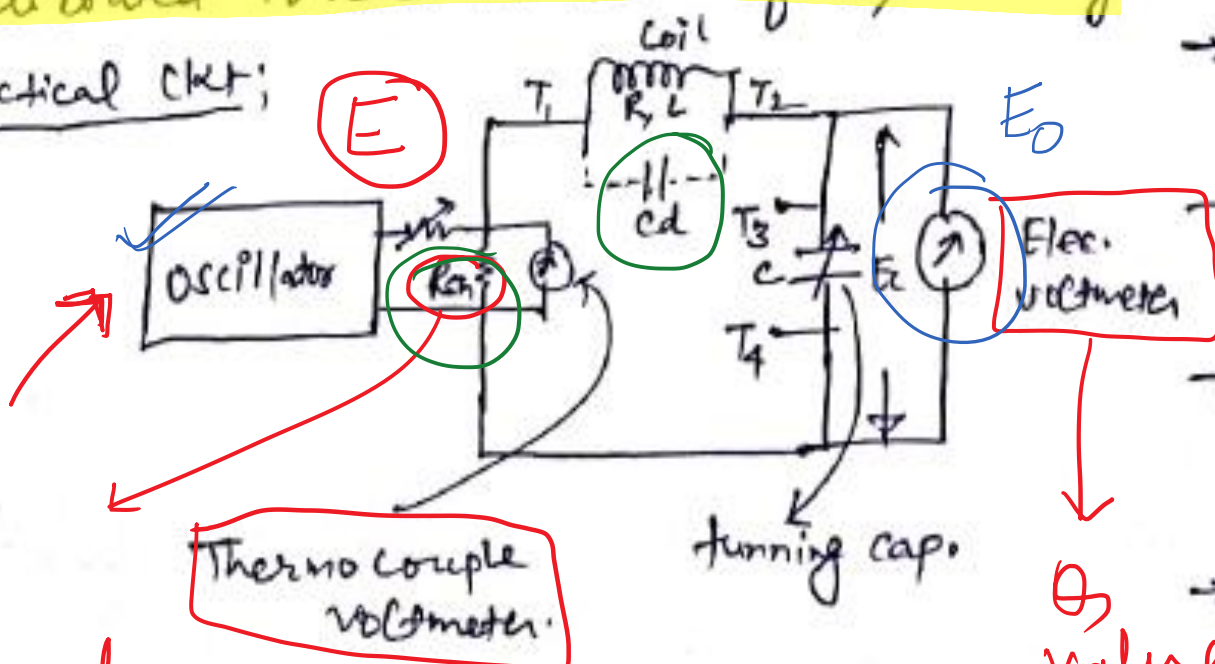

- Self contained variable freq oscillator
- deliver current to low value R_{sh}
- Through R_{sh} - small value of E injected into ckt.
- E is measured by a thermocouple voltmeter

R_{sh}
 low value
 (0.018 Ω)

$$Q_{Th} = \frac{\omega_0 L}{R}$$

Qmes

Applications:

- ① Measurement of Q: Oscillator set at desired freq. & then tuning cap. is adjusted for max. value of G_0 . Under this condition $Q = E_0/E$; if the voltmeter kept const., the voltmeter can be connected across the cap. may be calibrated to read Q directly.

The measured value is Q of whole ckt. not of the coil. Error caused on account of shunt resistance & also due to distributed cap. of ckt.

$$R_{sh} = \frac{1}{Y_p} = R_{eq}$$

$$Q_{meas} = \frac{\omega_0 L}{R + R_{sh}}$$

$$Q_{true} = \frac{\omega_0 L}{R}$$

$$Q_{true} = Q_{meas} \left(1 + \frac{R_{sh}}{R}\right)$$

Correction for distributed caps
↳ self cap.

$$Q_{true} = Q_{meas} \left(1 + \frac{C_d}{C}\right)$$

↻ R ↑
at low Q - neglected.
at high Q → can't neglect.
↳ R ↑

$R_{sh} = \text{Series Res.}$
 $C_d = \text{Self Cap.}$

$$Q_{\text{true}} = \frac{\omega_0 L}{R}$$

② Measurement of Inductance;

$$L = \frac{1}{4\pi^2 f_0^2 C}$$

③ Measurement of Effective Resistance;

$$R = \frac{\omega_0 L}{Q_{\text{true}}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

④ Measurement of self cap:

$$C_d = \frac{C_1 - n^2 C_2}{3}$$

$$f_1 = \frac{1}{2\pi\sqrt{L(C_1 + C_d)}}$$

C_1 = self cap

$$f_2 = \frac{1}{2\pi\sqrt{L(C_2 + C_d)}}$$

C_2 = self cap. or double f_{e1}

$$f_2 = 2f_1 \Rightarrow$$

$$C_d = \frac{C_1 - 4C_2}{3}$$

$$f_2 = n f_1$$

⑤ Measurement of B.W.:

$$Q = \frac{\omega_0}{\text{B.W.}}$$

$$\text{B.W.} = \frac{\omega_0}{Q} = \frac{2\pi f_0}{Q}$$

$L = ?$ $R = ?$

Example 2.10: When connected to a Q-meter an inductor is made to resonate at 400 kHz. The Q-factor of circuit is found to be 100 and the capacitance of Q-meter capacitor is set to 400 pF. Determine
(a) the inductance (b) the resistance of inductance.

Solution: Given $f_c = 400$ kHz

(a) At resonance $f_r = \frac{1}{2\pi\sqrt{LC}}$

$$2\pi f_r = \frac{1}{\sqrt{LC}}$$

$\Rightarrow L = \frac{1}{(2\pi f_r)^2 C}$

$$= \frac{1}{(2\pi \times 400 \times 10^3)^2 (400 \times 10^{-12})}$$
$$= 396 \mu\text{H}$$

$f_0 = 400 \text{ kHz}$
 $Q = 100$
 $C = 400 \text{ pF}$

(b) Q-factor at resonance = $\frac{2\pi f_r L}{R}$

$$R = \frac{2\pi f_r L}{Q}$$
$$= \frac{2\pi (400 \times 10^3) (0.396 \times 10^{-3})}{100}$$
$$= 9.95 \Omega$$

Ans. $P = 10^{-12}$

$Q = \omega_0 L$
 $\frac{Q}{R} = \frac{2\pi f_0 L}{R}$

Example 2.13: The self capacitance of a coil is measured by a Q meter. The circuit is set into resonance at 2 MHz and the tuning capacitor is at value of 460 pF. The frequency is now adjusted to 4 MHz and resonance conditions are obtained the tuning capacitor at 100 pF. Calculate the value of self capacitance of the coil.

$$C_d = \frac{C_1 - 4C_2}{3} = \frac{460 - 4 \times 100}{3} = 20 \text{ pF}$$

$$C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$$

$$f_1 = 2 \text{ MHz}$$

$$C_1 = 460 \times 10^{-12} \text{ F}$$

$$f_2 = 4 \text{ MHz}$$

$$C_2 = 100 \times 10^{-12} \text{ F}$$

$$n = f_2 / f_1$$

$$n = \frac{4}{2}$$

Example 2.17: To check the distributed capacitance of a coil it is resonated at 10 MHz with 120 pF and then is resonated at 15 MHz with 40 pF. What is the inductance of the coil and what is its equivalent distributed capacitance? [Raj.Univ. 2003]

Given - $f_1 = 10 \text{ MHz}$ $f_2 = 15 \text{ MHz}$
 $C_1 = 120 \text{ pF}$ $C_2 = 40 \text{ pF}$

$$n = f_2 / f_1 = \frac{15}{10} = 1.5$$

$$C_d = \frac{C_1 - n^2 C_2}{n^2 - 1} = \frac{120 \times 10^{-12} - (1.5)^2 40 \times 10^{-12}}{(1.5)^2 - 1}$$
$$= \underline{\hspace{2cm}}$$

Example 2.17: To check the distributed capacitance of a coil it is resonated at 10 MHz with 120 pF and then is resonated at 15 MHz with 40 pF. What is the inductance of the coil and what is its equivalent distributed capacitance? [Raj.Univ. 2003]

$f_1 = 10$
 $f_2 = 15$

Solution:

$$L = \frac{1}{(2\pi f)^2 C} = \frac{1}{(2\pi \times 10 \times 10^6)^2 \times 120 \times 10^{-12}} = 2 \times 10^{-6} \text{ H}$$

If C_d is the distributed capacitance,

$$\Rightarrow f_1 = \frac{1}{2\pi\sqrt{L(C_1 + C_d)}}$$

and $f_2 = \frac{1}{2\pi\sqrt{L(C_2 + C_d)}}$; $f_2 = 1.5f_1$

$$\therefore \frac{1}{2\pi\sqrt{L(C_2 + C_d)}} = \frac{1.5}{2\pi\sqrt{L(C_1 + C_d)}}$$

$$\therefore \frac{1}{C_2 + C_d} = \frac{2.25}{C_1 + C_d} \Rightarrow 1.25C_d = C_1 - 2.25C_2$$

or in general, $C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$ where n - integral ratio of frequencies.

Substituting the values of C_1 and C_2 then

$$C_d = \frac{120 - 2.25 \times 40}{1.25} = \frac{30}{1.25} = 24 \text{ pF}$$

$f_2 = 2f_1$
 $n = f_2/f_1$
 $C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$
 $\frac{15}{10} = 1.5$

$$C_d = \frac{C_1 - 4C_2}{3}$$

Example 2.16: A coil with a resistance of 3Ω is connected to the terminals of a Q meter. Resonance occurs at an oscillator frequency of 5 MHz with a capacitance of 100 pF. Calculate the percentage of error introduced by the insertion resistance $R_{sh} = 0.1\Omega$

[Raj. Univ. 2003]

$$R = 3\Omega$$

$$f_0 = 5 \times 10^6 \text{ Hz}$$

$$C = 100 \times 10^{-12} \text{ F}$$

$$R_{sh} = 0.1\Omega$$

$$L = \frac{1}{(2\pi f_0)^2 C}$$

$$Q_{true} = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$$

$$Q_{mes} = \frac{\omega_0 L}{R + R_{sh}}$$

$$\% \text{ error} = \frac{Q_{true} - Q_{mes}}{Q_{true}} \times 100$$

Example 2.16: A coil with a resistance of 3Ω is connected to the terminals of a Q meter. Resonance occurs at an oscillator frequency of 5 MHz with a capacitance of 100 pF. Calculate the percentage of error introduced by the insertion resistance $R_{sh} = 0.1\Omega$

[Raj.Univ. 2003]

Solution: $f = \frac{1}{2\pi\sqrt{LC}}$

or $L = \frac{1}{(2\pi f)^2 C}$

$$L = \frac{1}{(2\pi \times 5 \times 10^6)^2 \times 100 \times 10^{-12}} = 10.13 \mu H$$

$$Q_{actual} = \frac{\omega L}{R} = \frac{2\pi \times 5 \times 10^6 \times 10.13 \times 10^{-6}}{3} = 106.08$$

Done ✓

With insertion resistance $R_{sh} = 0.1\Omega$

$$Q_{observed} = \frac{\omega L}{R + R_{sh}} = \frac{2\pi \times 5 \times 10^6 \times 10.13 \times 10^{-6}}{3.1} = 102.66$$

$$\% \text{ error} = \frac{106.08 - 102.66}{106.08} \times 100 = 3.2$$

$$\frac{Q_{act}}{Q_{obs}} = \frac{R + R_{sh}}{R} = 1 + \frac{R_{sh}}{R}; \quad Q_{act} = Q_{obs} \left(1 + \frac{R_{sh}}{R} \right)$$

To make observed value as near as Q_{actual} , R_{shunt} should be as small as possible.




Grounding: Ground is the reference point in an electrical circuit from which other voltages are measured.

② A common return path for electrical current.

③ A direct physical connection to the earth.


* earth is electrically neutral → considered at zero potential
↳ ref point for voltage measurement.

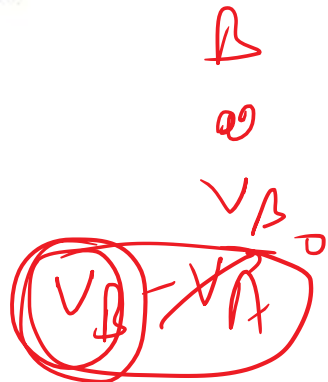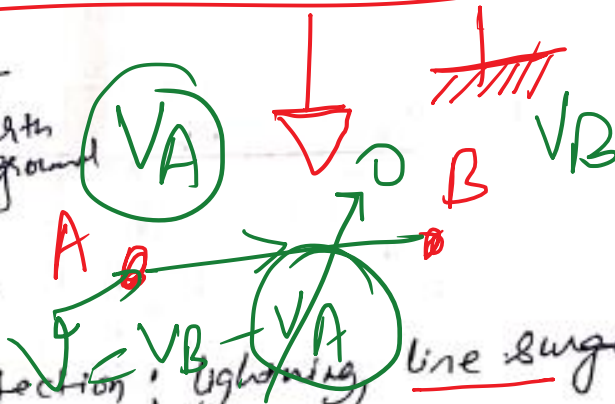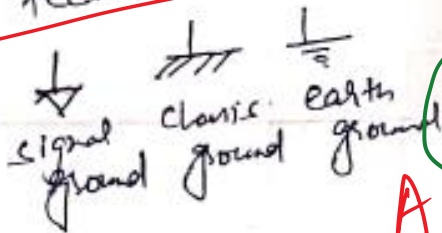A true earth ground physically consists of a conductive pipe or rod driven in to a min. depth of 3 feet.



Purpose of grounding:

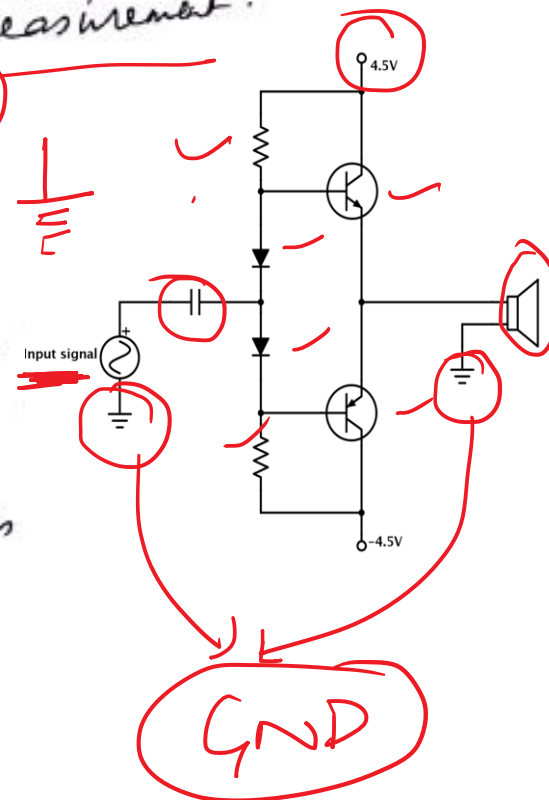- (i) over voltage protection; lightning, line surges
- (ii) voltage stabilization
- (iii) over current protection.




Shielding:

It can be defined as the placing of sensitive electronic parts & components in a metal casing to prevent electric & magnetic fields entering in that case.

eg. - use to block electrostatic & magnetic interference
↳ Co-axial cable

~~Characteristics~~ Characteristics of good shielding ✓

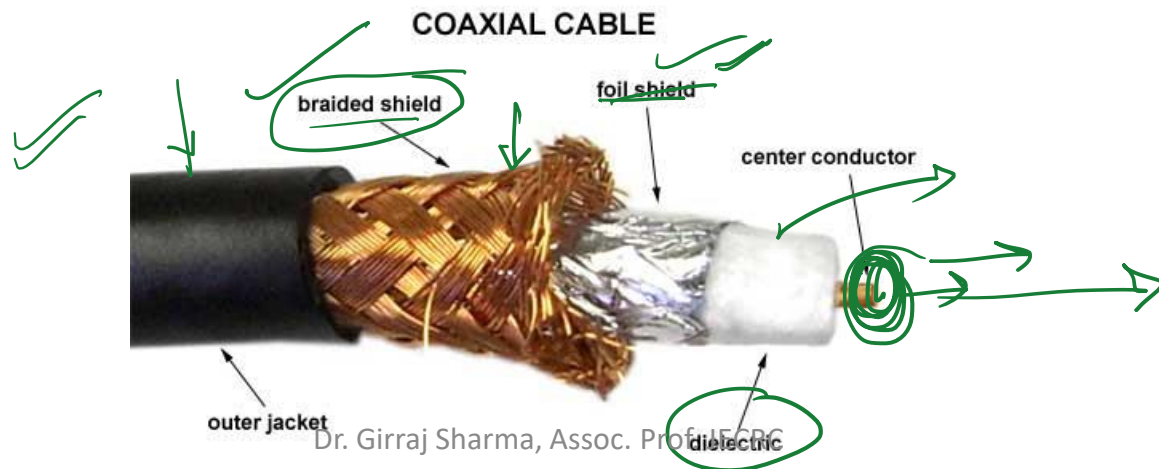- it must confine undesired signal generated within case
- The shielding material must have low surface impedance
good electrical continuity
- It must prevent equipment from receiving undesired signal





Vector impedance meter

- The vector impedance meter is used to measure impedance of unknown component over a wide frequency range & simultaneously it determines the phase angle.
- The quality of component whether is inductive or capacitive or resistive can be determined by determining phase difference between the voltage across the component & current through component.
- The component whose impedance magnitude and phase angle to be measured is simply connected across the input terminals of the instrument.
- The desired frequency is selected by tuning the front panel control.
- There are two indicators to indicate the magnitude and the phase angle.

Because two quantities (magnitude and phase angle) have to be measured, the two principles are used.

Vector Impedance Meter

$$Z = \frac{V}{I}$$

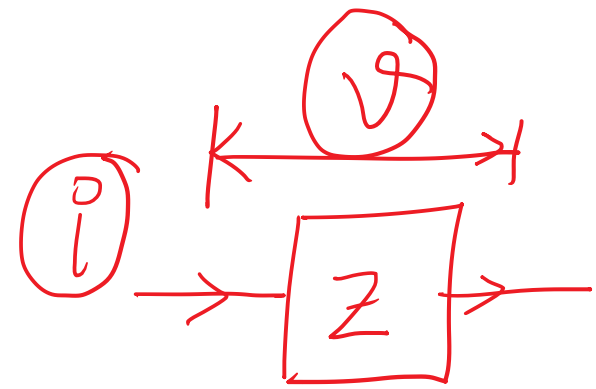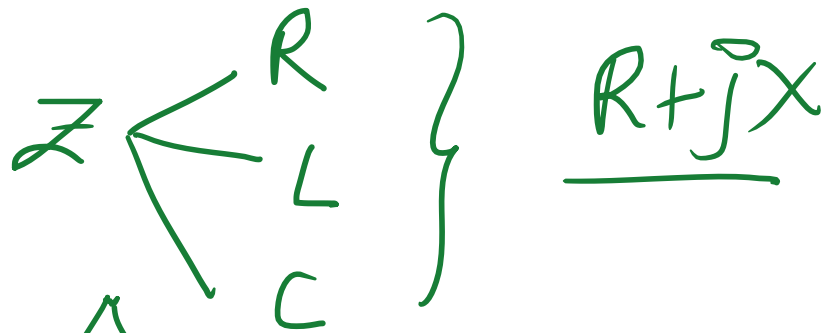

mag. Phase Angle

V — phase diff.
 I —

Constant current mode Constant voltage mode

Vector impedance meter



Mag. + Phase Angle

CCM CVM

Range Frequency

Wien Bridge Oscillator


Automatic Gain Control with Feedback

AGC

Impedance Range Switch

Voltage → CCM

Current

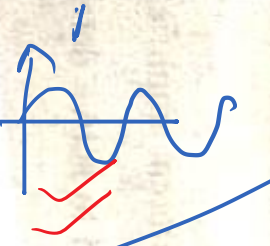


CCM → 1, 10, 100

CVM → 1K, 10K, 100K

1M

90°

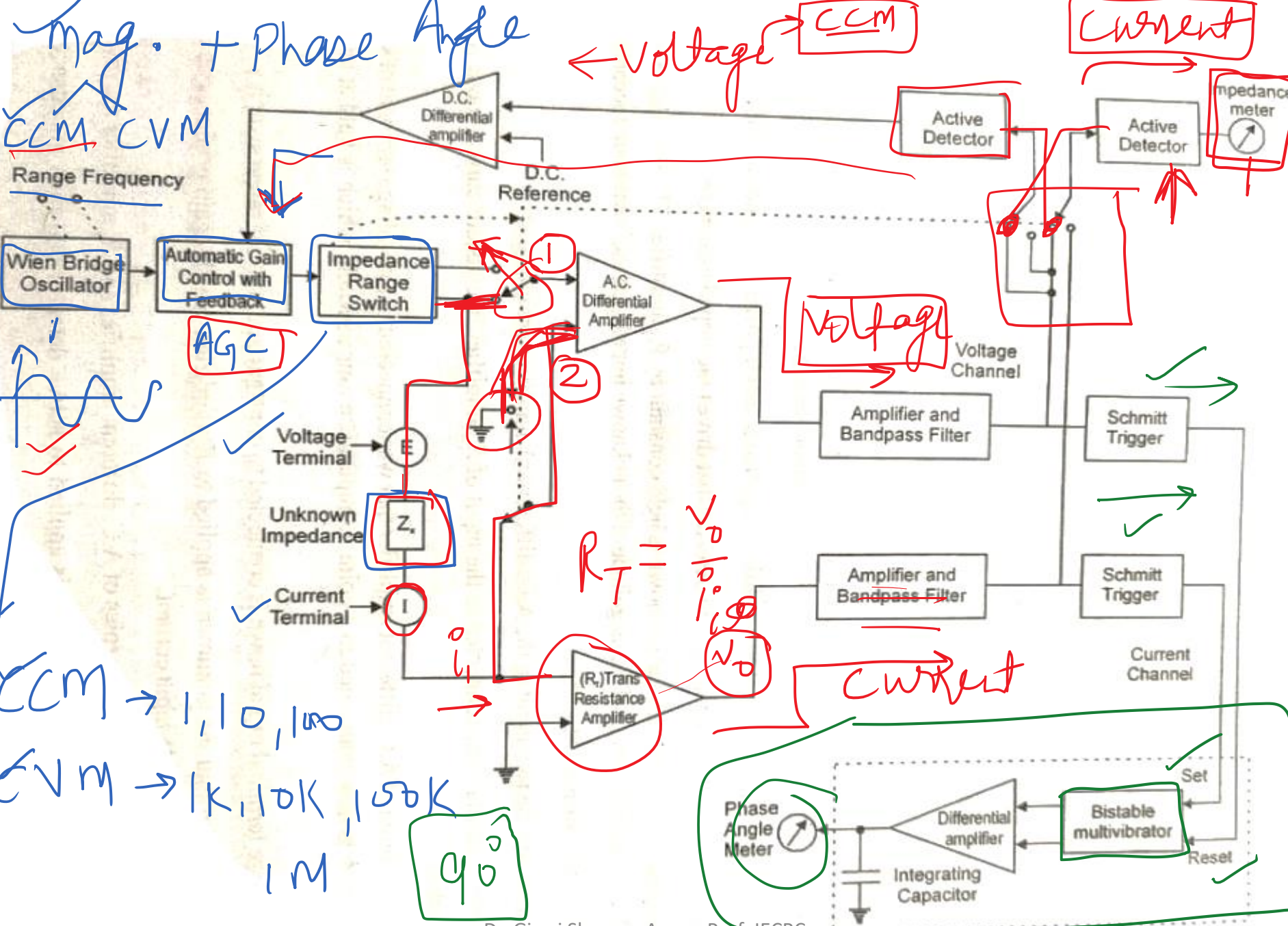

$$R_T = \frac{V_0}{I_0}$$

Phase detector circuit

- Magnitude is determined by measuring the current through the unknown component when a known voltage is applied across it or by measuring the voltage across the component when a known current is passed through it.
- The block diagram of vector impedance meter is shown in the figure 2.26.
- In this a wein bridge oscillator is used as signal source, which can produce different frequency signals.
- The signal is fed to AGC amplifier (automatic gain control), which allows accurate gain adjustment by means of feedback voltage.
- The gain is adjusted by impedance range switch.
- The impedance range switch is a precise attenuator network which controls the output voltage of oscillator.

The impedance range switch operates in two modes.

1. Constant current mode (three lower ranges X1, X10 and X100).
2. Constant voltage mode (four higher ranges X 1K, X 10K, X 100K and X 1M)

(a) Constant Current Mode

- In this mode the unknown component is connected to the input of A.C. differential amplifier.
- The current supplied to the unknown component is decided by setting of range switch.
- This supplied current is held constant by the action of trans-resistance of R_T amplifier.
- R_T amplifier converts the current through the unknown impedance into a voltage output.
- The output voltage is proportional to the supplied input current.
- The output of R_T amplifier is fed to the amplifier and Band pass filter.
- Band pass filter consists of low and high band filters, which restricts the amplifier bandwidth.
- This output of band pass filter is fed to active detector and D.C. differential amplifier.
- The D.C. differential amplifier compares the input with a D.C. reference voltage.
- The output of D.C. differential amplifier is fed to AGC amplifier to regulate the gain of AGC amplifier and hence the voltage applied to the range switch.
- The output of A.C. differential amplifier is applied to an amplifier and band pass filter.
- The output of filter is connected to detector that drives the impedance meter.
- Since the current through the unknown is held constant by R_T amplifier. The impedance meter deflects in the proportion of the magnitude of the unknown impedance and it calibrated accordingly.

(b) Constant Voltage Mode

- In this mode the two input to the A.C. differential amplifier are changed.
- The terminal that was connected to the input of R_f amplifier in constant current mode is now grounded.
- The other input of A.C. different amplifier that was connected to the voltage terminal of known impedance is now connected to a point in impedance range switch, which is held at constant potential.
- The voltage terminal of unknown is connected to constant potential of range switch.
- The current through the unknown is applied to R_f amplifier, which again produces an output voltage proportional to input current.
- In constant voltage mode, the roles of A.C. different amplifier and R_f amplifier are reversed.
- The voltage output of R_f amplifier is applied to active detector and then impedance meter through amplifier and band pass filter.
- The output voltage of A.C. differented amplifier controls the gain of AGC amplifier in the same manner that the R_f amplifier did in the constant current mode.


Radio freqⁿ → High freqⁿ

2.8.2 R.F. Power Measurements

- There are various methods of R.F. power measurement. One of the most popular method is bolometer method.
- In this method, the unknown power is absorbed in a specially constructed bolometer element of resistive element.
- The resultant temperature rise is then detected by measuring the change in bolometer resistance by means of an auxillary bridge circuit.
- The bolometer element may consist of normal resistive element with a positive temperature coefficient or thermistors which has negative temperature coefficient made up of metallic oxide materials.
- Here the radio frequency power enters from a coaxial line.
- The bypass capacitor provides a return path for the R.F. current and an insulated connection to the bolometer.

$$\text{Power} = I \cdot V$$

Thermistor / thermocouple RTD

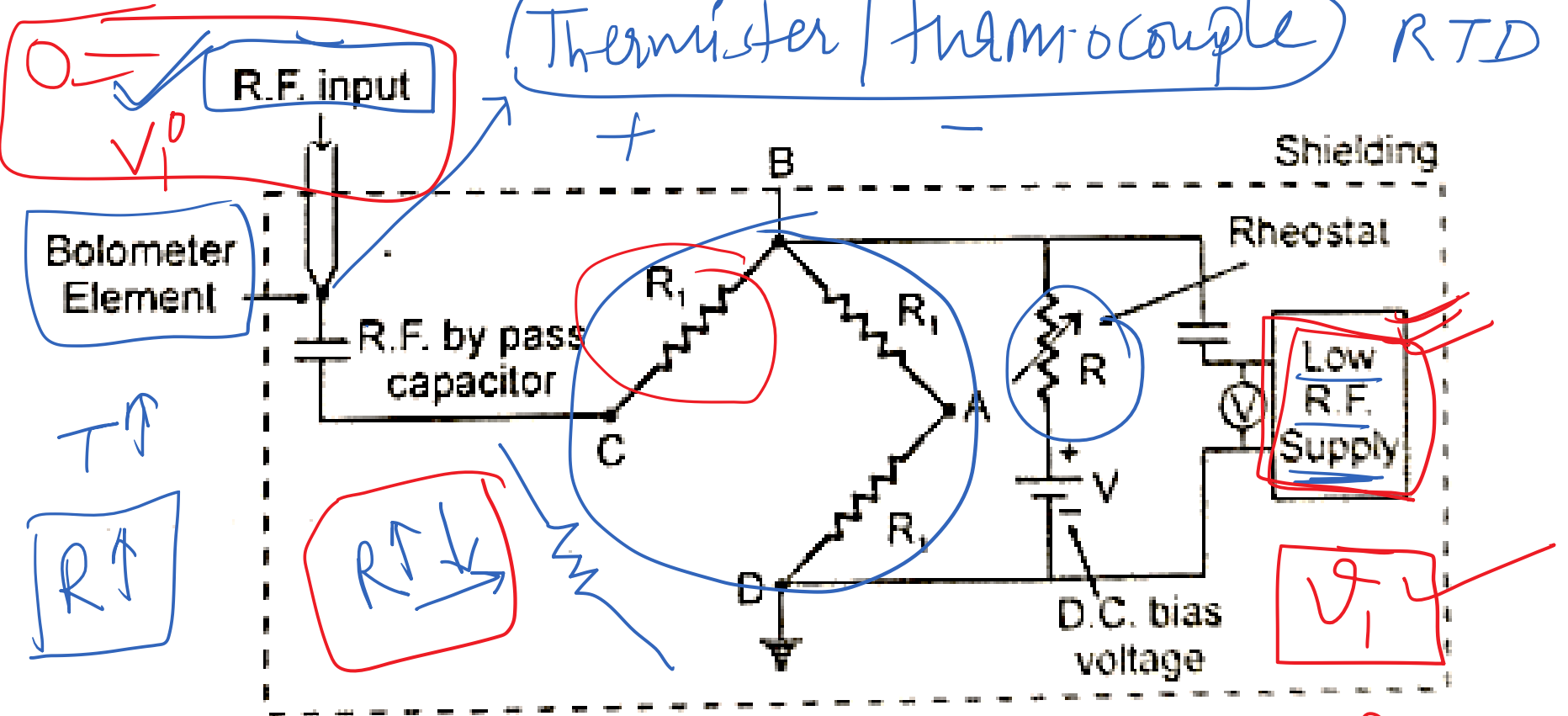

$T \uparrow$
 $R \uparrow$

$R \uparrow \downarrow$



$$P/Q = R/S$$

- The resistance change in the bolometer is measured with the bridge ABCD.
- The arm CD is supplied by the resistance of bolometer element.

The bridge simultaneously excited by direct current from voltage V and by a low R.F.

The D.C. current is adjusted by rheostat R until bridge is balanced.

At balance condition measure the voltage V_1 of low R.F. supply

Now turn off the R.F. power, the bridge again unbalanced.

The balance is again restored by increasing the power from low R.F. supply.

Now measure the voltage V_2 of low RF power is

The radio frequency power is



$$= \frac{V_2^2 - V_1^2}{4R_1}$$

The lead from bolometer to the bridge is shielded to avoid stray fields from radio and low frequency into the system.

Range & Resolution of digital volt -
meter
Resolution
least
Count

↳ Seven Segment LED.

3 digit display

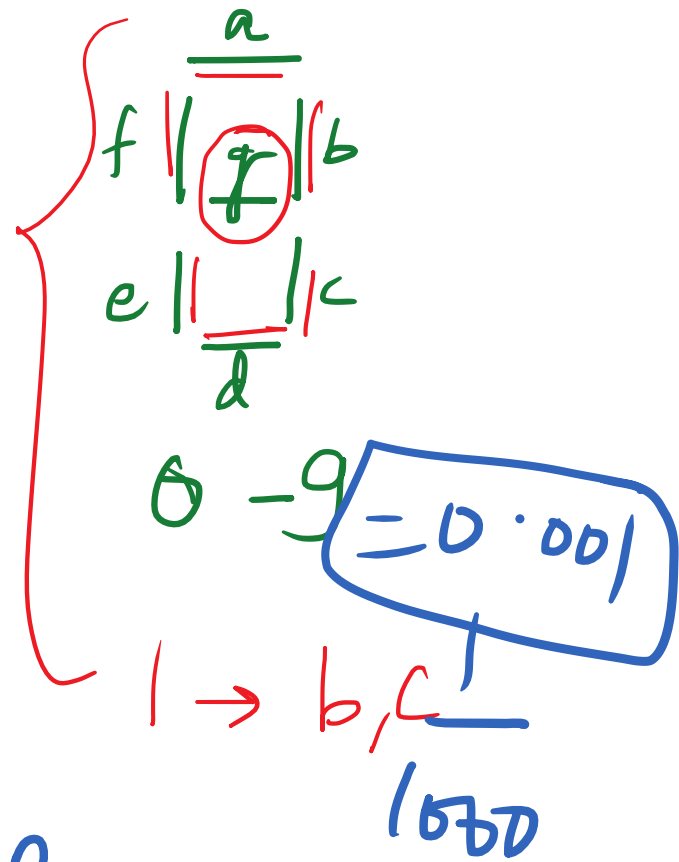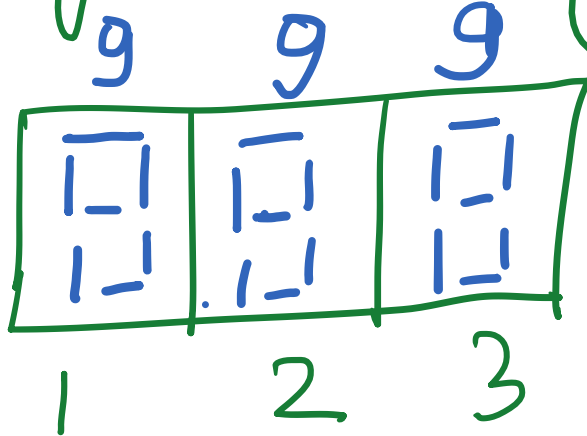

① Reset count - 000

② Min. Count - 001

③ Max. Count - 999

Total count = 1000

Resolution
Resolution


$$= \frac{1}{10^N}$$

$$N = 3$$

$N =$ No. of full digit

$$\text{Resolution} = \frac{\text{Range}}{10^N}$$

$N = \text{No. of full digit}$

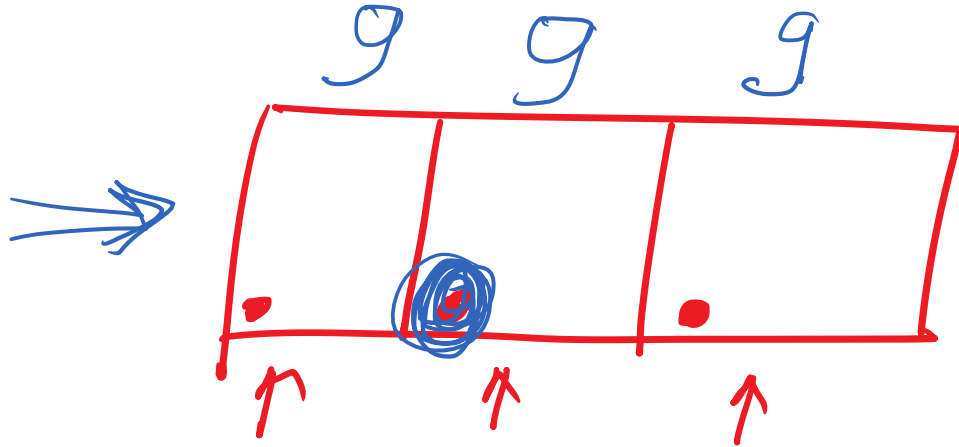


$$R = \frac{10}{10^3} = 0.01 \text{ } 10\text{m}\Omega$$

Reset count 000

min count $0.01 = 10\text{m}\Omega \Rightarrow$ least count



max count = $9.99 = 10 \text{ V}$ Range

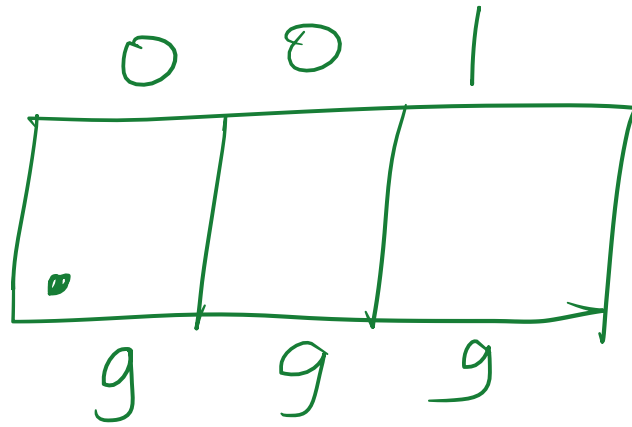

min. count 0.001 = 1m ✓

max count 0.999 = 1 ✓

Range Extension

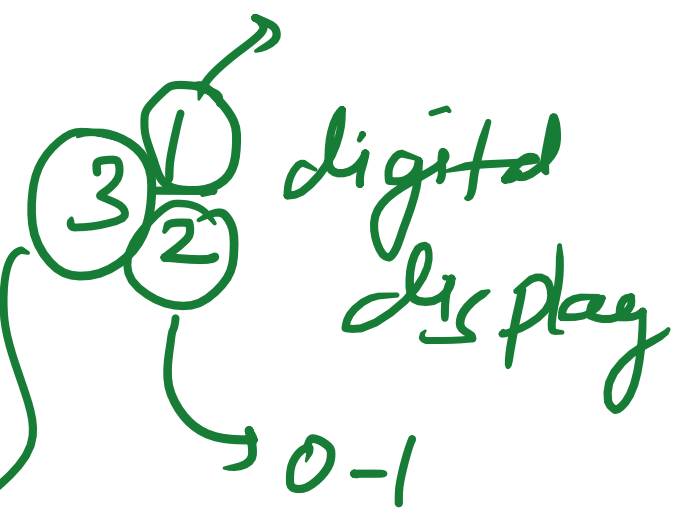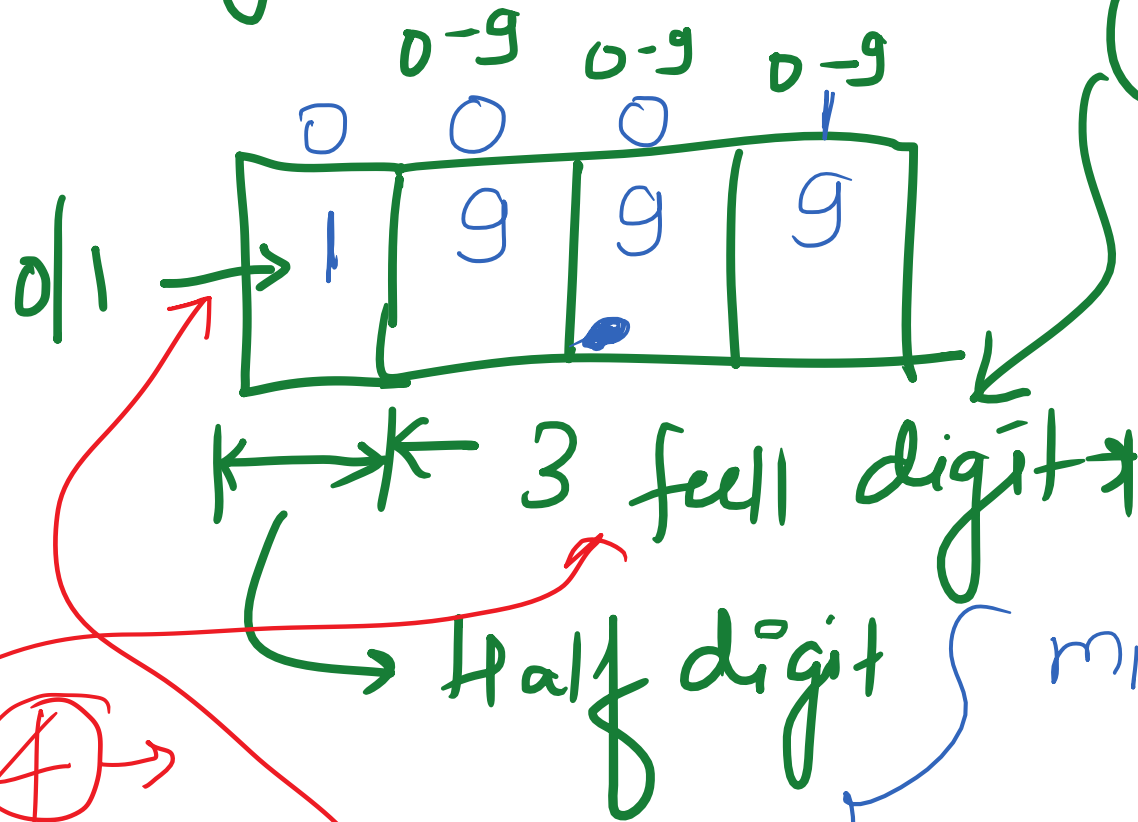

min count
= 0.01
max count 19.99
⇒ 20V

Example 2.14: A $4\frac{1}{2}$ digit voltmeter is used for voltage measurements. Find :

(i) Its resolution

(ii) How 12.98 V will be displayed on a 10 V range?

(iii) How 0.6973 will be displayed on 1V and 10V ranges?

[R.T.U. 2008]

Solution: (i) Resolution = $\frac{1}{10^n} = \frac{1}{10^4} = 0.0001$

where the number of full digits is $n = 4$

(ii) there are 5 digit places in $4\frac{1}{2}$ digit, therefore 12.98 should be displayed as 12.980.

Resolution on 1V range is $1V \times 0.0001 = 0.0001$ any reading upto the 4th decimal can be displayed. Hence 0.6973 will be displayed as 0.6973.

(iii) Resolution on 10V range = $10V \times 0.0001 = 0.001V$ hence the third decimal up to 3rd decimal places can be displayed. Therefore on a 10V range, the reading will be 0.697 instead of 0.6973.