

Co-5: Design Custom/ASIC design using FPGA kit through VHDL code.

Learning Outcomes (LO)

Students will able to learn

LO-1 : Various ECAD Tools.

LO-2 : Front End and Back End Design of VLSI Circuits.

LO-3: Custom ASIC Designs.

LO-4 : VHDL Code of following

- 1) Logic Gates.
- 2) Flip –Flops
- 3) Shift Register.

VLSI DESIGNING :-


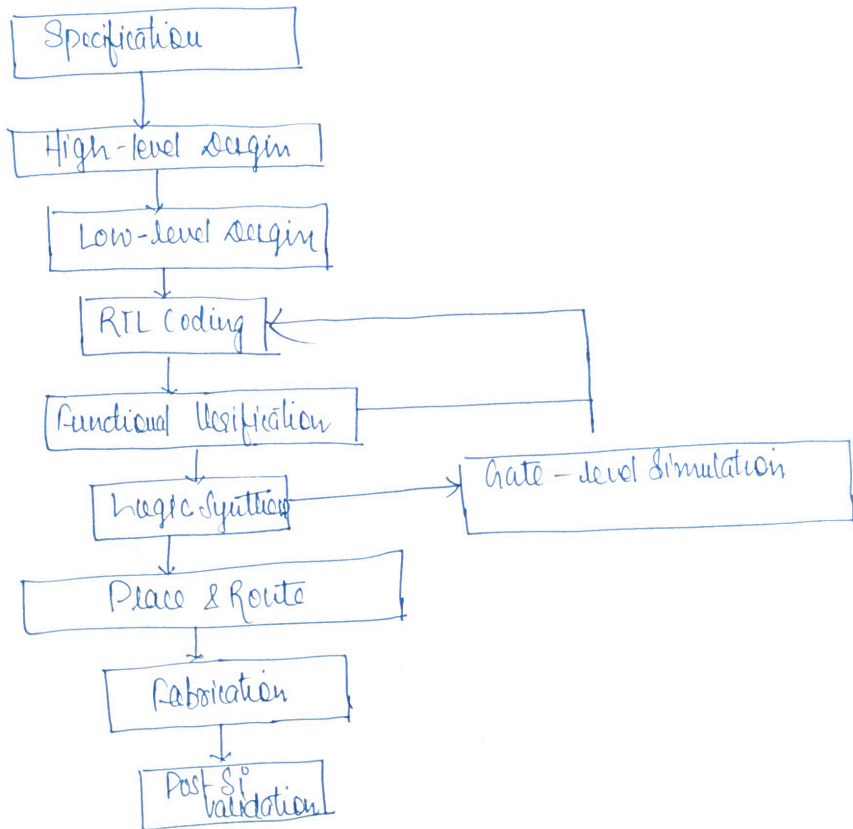
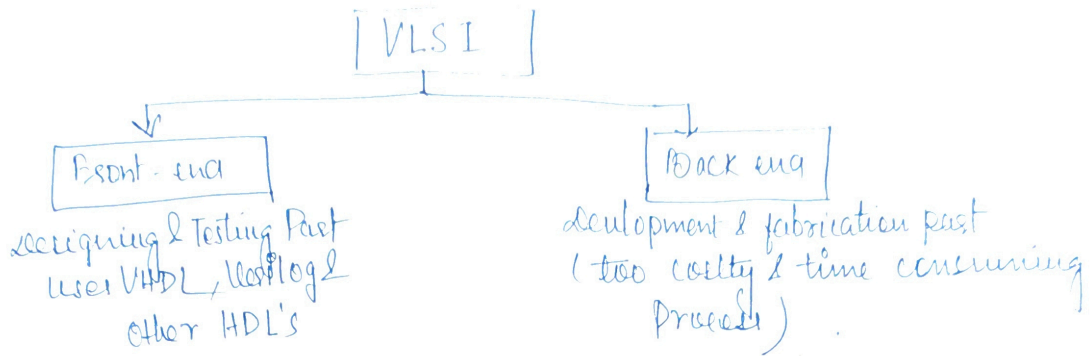


Fig: Block diagram of VLSI design - Front End & Back end.

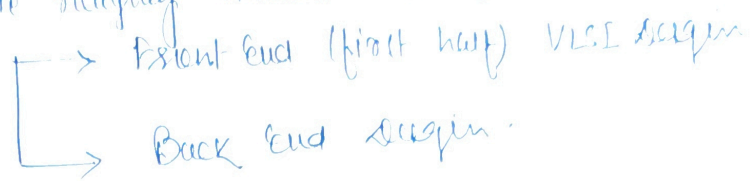The above stages are roughly divided into 2 halves.



Front End VLSI Design :-

All stages from specification to functional verification are normally considered as a part of front end and engineers working on any of these are front end VLSI design engineers.

Back End VLSI Design :-

All stages from logic synthesis till fabrication are considered as a back end engineer.

1) SPECIFICATION :-

In the design process we define important parameters of the system that has to be designed into specification.

2) High level design :-

In this various details the design architecture are defined. In this stage, details about the different functional blocks & interface communication protocols between them are defined.

3) low-level design :-

This phase is known as Microarchitecture phase.

In this phase lower level design details about each functional blocks implementation are designed.

This include details like modules, state machine, internal registers decoder, etc.

RTL CODING :-

In RTL coding, the micro design is modelled in a hardware description language like Verilog/VHDL using constructs of language.

Synthesizable constructs are used so that the RTL model can be input to a synthesizer tool to map the design to actual gate level.

FUNCTIONAL VERIFICATION :-

Process of verifying the functional characteristics of design by generating different input stimuli & checking for correct behaviour of design implementation.

LOGIC SYNTHESIS :-

Synthesis is a process in which synthesizer tools like compiler takes in RTL, target technology and constraints as input maps the RTL to target technologies.

PLACEMENT & ROUTING :-

Gate level net list from synthesizer tool is taken and imported into place & route tool in Verilog netlist format.

All these gate & flip-flop are placed, clock tree synthesized & routed. After this each block is routed, Output of P&R tool is a GDS file which is used by foundry for fabricating IC.

GATE LEVEL SIMULATION :-

The placement & Routing tool generates an SDF (Standard Delay File) that contains timing information of the gates.

This is back annotated along with gate level netlist & some functional patterns are run to verify the design functionally.

A static timing analysis tool like prime time can also be used for performing static timing analysis checks.

FABRICATION :-

Once the gate level simulation verify the functional correctness of gate level design after placement & Routing phase, the design is ready for manufacturing.

The final ADS file (a binary database) is normally sent to a foundry which fabricates the silicon. Once fabricated proper packaging is done.

POST SILICON FABRICATION :-

Once the chip is back from fabrication it need to be test in real environment and tested before using in market.

This phase involves testing in LAB using hardware board & software / firmware that programs the chip.

Since the speed of simulation with RTL is very slow compared to testing in LAB with real silicon, there is always a possibility to find a bug in silicon validation & hence is very important.

Custom ASIC YIELDING:

- ⇒ Custom design is a methodology for designing integrated circuits by specifying the layout of each individual transistors and the interconnections between them.
- ⇒ Custom design includes various forms
 - ↳ Full Custom
 - ↳ Semi Custom

Level CUSTOM :-

- Full Custom design methodology for designing integrated circuits by specifying the layout of each individual transistors & interconnections between them.
- ⇒ Full Custom design include various form of semi-Custom design.
- ⇒ Full Custom design potentially maximizes the performance of chip minimizes its area, but is extremely labor intensive to implement. Full custom design is limited to ICs that are able to fabricate in extremely high volume volumes notably certain microprocessors and small numbers of ASICs.
- ⇒ Full Custom design requires all the components to be designed & verified right from transistor level.
- ⇒ In Full Custom design
 - * Some (possibly all) logic cells are customized and mask layers are customized.
- ⇒ In Full Custom design all layers are optimized for an embedded system's particular digital implementation.
 - * placing transistors
 - * sizing transistors


* Routing holes.

Advantages

- * High design & layout design effort
- * Each circuit elements carefully handcrafted
- * Full custom is usually for large volume product
- * Typically used for high-volume applications
- * Excellent performance, small size, low power.

Disadvantages

- * High NRE cost
- * long time to come in market

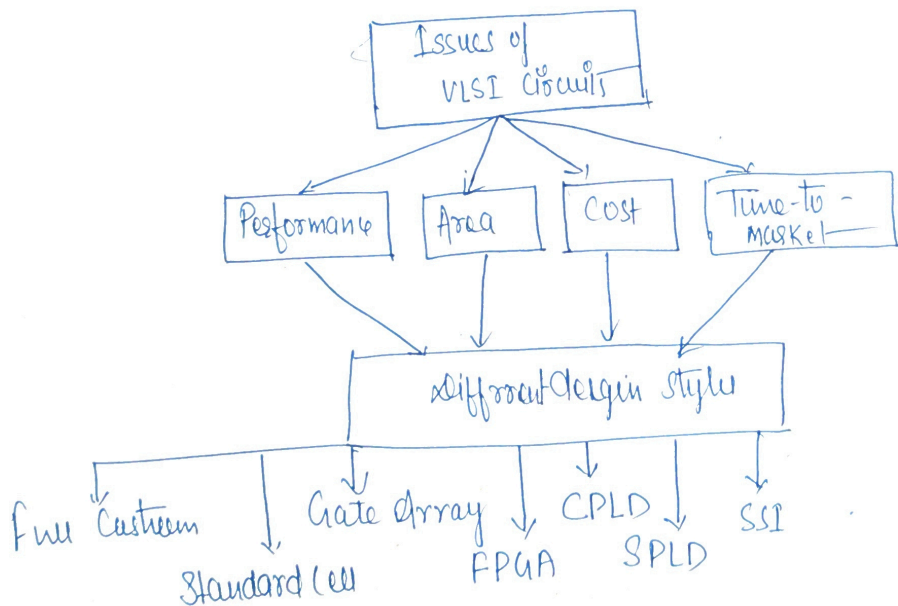

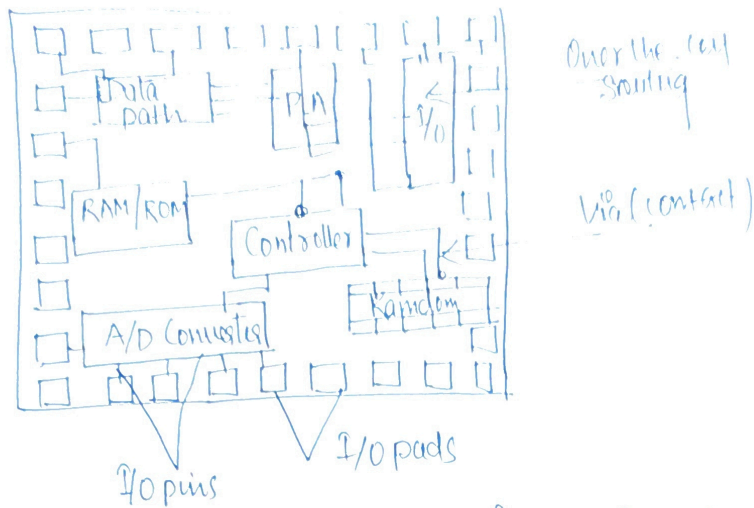


Fig: Block Diagram of Full Custom design

SEMI-CUSTOM ASIC DESIGN:-

In Semi-Custom all logic cells are pre-designed (defined in cell library) and some (possibly all) of the mask layers are customized.

Semi-Custom ASIC DESIGN

- Standard-cell based
- Gate-Array based ASICs.

Standard cell based:-

- Characteristics of standard cell based design
- ⇒ The chip layout can be created automatically by CAD tools because of regular arrangements of logic gates (cells) in rows.
 - ⇒ Standard cells can be placed anywhere on a silicon


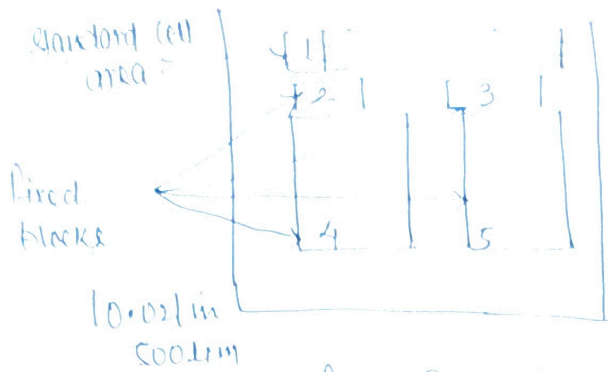


Fig: Block diagram of standard cell

 3)

⇒ Standard-cell area can be used in communication with larger pre-designed cells (microcontroller, microprocessor), known as mega-cells.

⇒ Standard-cells are designed to fit horizontally together to form rows.



⇒ 25 microns wide (lambda is 0.25)

AB: abutment box

BB: Bounding box

Power supplies: VDD, GND

Each different shaded & labeled pattern represents a

different layer

Connections: A1, B1, C

GATE - ARRAY :-

⇒ Gate Array is an approach to design & manufacture of application specific integrated circuits (ASICs) using a prefabricated chip with components that are later interconnected into logic device (e.g. NAND gates, flip-flop).

⇒ Gate Array have also known as Uncommitted Logic Array (CPLAs) & Semi-Custom chips.

⇒ Gate array ranks second after Gate Array design (GA) ranks second after the FPGA, in terms of fast prototyping capability.

⇒ Gate Array requires a two-step manufacturing process.

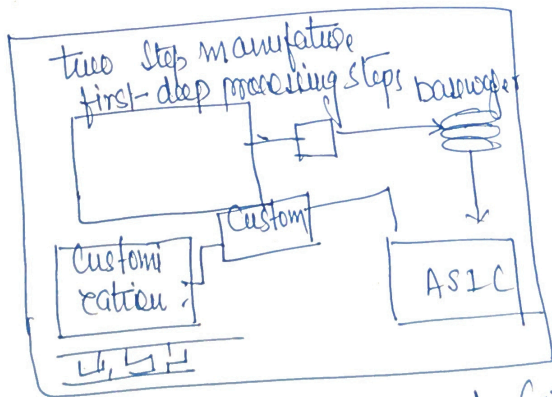




Fig: Block diagram of Gate Array.

INTRODUCTION


Design of various Logic Gates using VHDL

LOGIC GATES:



A logic gate performs a logical operation on one or more logic inputs and produces a single logic output. The logic normally performed is Boolean logic and is most commonly found in digital circuits. Logic gates are primarily implemented electronically using diodes or transistors, but can also be constructed using electromagnetic relays (relay logic), fluidic logic, pneumatic logic, optics, molecules, or even mechanical elements.

  

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

 


INPUT		OUTPUT
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

  


INPUT		OUTPUT
A		NOT A
0		1
1		0

 In electronics a NOT gate is more commonly called an inverter. The circle on the symbol is called a *bubble*, and is generally used in circuit diagrams to indicate an inverted (active-low) input or output.




INPUT		OUTPUT
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0


VLSI DESIGN LAB (7EC4-21)

 

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

 

INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

 

INPUT		OUTPUT
A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

Program:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity all_ga is  
  Port ( a : in STD_LOGIC;  
        b : in STD_LOGIC;  
        c : out STD_LOGIC;  
        c1 : out STD_LOGIC;  
        c2 : out STD_LOGIC;  
        c3 : out STD_LOGIC;  
        c4 : out STD_LOGIC;  
        c5 : out STD_LOGIC;  
        c6 : out STD_LOGIC);  
end all_ga;
```


```
architecture Behavioral of all_ga is
```

```
begin  
  c <= a and b;  
  c1 <= a or b;  
  c2 <= a nand b;  
  c3 <= a nor b;  
  c4 <= a xor b;  
  c5 <= a xnor b;  
  c6 <= not b;
```

```
end Behavioral;
```

OUTPUT:

RTL View

 


Aim : Design a RS & JK flip-flop

RS & JK FLIP-FLOP

RS flip-flops are useful in control applications where we want to be able to set or reset the data bit. However, unlike SR latches, SR flip-flops change their content only at the active edge of the clock signal. Similar to SR latches, SR flip-flops can enter an undefined state when both inputs are asserted simultaneously.

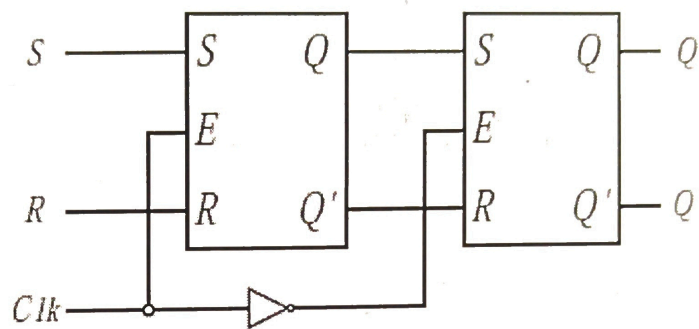The truth table and circuit diagram are as follows:



S	R	Q	Q_{next}	Q_{next}'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	×	×
1	1	1	×	×

Program:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

```



```

entity SR-FF is
PORT( S,R,CLOCK,CLR,PRESET: in std_logic;
      Q, QBAR: out std_logic);
end SR-FF;

```

```

Architecture behavioral of SR-FF is
begin
P1: PROCESS(CLOCK,CLR,PRESET)
variable x: std_logic;
begin
if(CLR='0') then
x:='0';

elsif(PRESET='0')then
x:='1';

elsif(CLOCK='1' and CLOCK'EVENT) then

if(S='0' and R='0')then
x:=x;
elsif(S='1' and R='1')then
x:='Z';

elsif(S='0' and R='1')then
x:='0';


else
x:='1';

end if;
end if;

Q<=x;
QBAR<=not x;
end PROCESS;
end behavioral;

```

Simulation Waveforms

 


JK FLIP-FLOP

JK flip-flops are very similar to SR flip-flops. The J input is just like the S input in that when asserted, it sets the

flip-flop. Similarly, the K input is like the R input where it clears the flip-flop when asserted. The only difference is when both inputs are asserted. For the SR flip-flop, the next state is undefined, whereas, for the JK flip-flop, the next state is the inverse of the current state. In other words, the JK flip-flop toggles its state when both inputs are asserted.

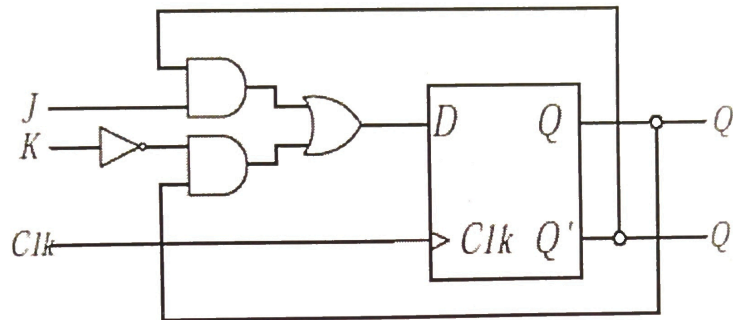The truth table and circuit diagram are drawn below:



J	K	Q	Q_{next}	Q_{next}'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

Program:

```

-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity JK-FF is
PORT( J,K,CLK,PRST,CLR: in std_logic;
      Q, QB: out std_logic);
end JK-FF;
```

Architecture behavioral of JK-FF is

```

begin
P1: PROCESS(CLK,CLR,PRST)
variable x: std_logic;
begin
if(CLR='0') then
x:='0';

elsif(PRST='0')then
x:='1';


elsif(CLK='1' and CLK'EVENT) then
if(J='0' and K='0')then
x:=x;
elsif(J='1' and K='1')then
x:= not x;

elsif(J='0' and K='1')then
x:='0';
else
x:='1';

end if;
end if;
Q<=x;
QB<=not x;
end PROCESS;
end behavioral;

```

Simulation Waveforms

 

Quiz Questions with answer.

Aim:- To Design a 8 bit shift register


8-bit Shift Register

Shift Register is a type of sequential circuit formed by combination of flip-flops and is capable of shifting data from left to right or vice-versa. Shift register basically performs two functions:

- i. Shifting of data(Transfer of data)
- ii. Storage function

The circuit diagram for 8-bit Shift Register is given as:

Logic Diagram

 

The vhdl program for 8-bit shift-left register with a positive-edge clock, serial in, and serial out.

Program:

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity shift is  
port(C, SI : in std_logic; SO : out std_logic);  
end shift;
```

```
architecture archi of shift is  
signal tmp: std_logic_vector(7 downto 0);
```

```
begin  
process (C)  
begin  
if (C'event and C='1') then  
for i in 0 to 6 loop
```

```

tmp(i+1) <- tmp(i);
end loop;
tmp(0) <- S1;
end if;
end process;

S0 <= tmp(7);
end archi;

```

Simulation Waveforms

